 


### Building an Adder

- We will build a full adder



- First, a description of the entity:  


```
library ieee;
use ieee.std_logic_1164.all;
entity full_adder is
    port (
        x, y, z : in std_logic;
        s, c    : out std_logic;
    );
end full_adder
```
- Now, a behavioural description  
Architecture behav of full\_adder is  
Begin  
 FA: process (x, y, z)  
 Variable tmp: std\_logic;  
 Begin  
 Tmp:= X xor Y;  
 S<= tmp xor Z after 3 ns;  
 C<= (X and Y ) or (Z and tmp) after 5 ns;  
 End process;  
End behave;
- Tmp is a variable
  - Variables aren't signals
  - Used like variables in a programming language –to hold info
  - Variables have nothing to do w/ structural descriptions or in circuits
  - Assignment to a variable is done with `=` NOT `<=`
- The sequential statements execute in order

- The circuits total  $T_{pol}$  (propagation delay is 5 ns;
- The assignments execute at the same simulation time
- The “after” just delays the result

– Now, a structural description:

- First, we need gates:
  - and\_gate
  - xor\_gate
  - or\_gate
- now, we can build a half adder:
 

```
entity half_adder is
    port(
        x, y: in std_logic;
        s, c: out std_logic
    );
end half_adder;
architecture struct of half_adder is
    begin
        XOR1: entity work.xor_gate
            port map (
                a=>x,
                b=>y,
                c=>s);
        AND1: entity work.adn_gate
            port map(
                a=>x,
                b=>y,
                c=>c);
    end struct
```

 

- “struct” is the name of this implementation
- “XOR1” and “AND1” are the labels for the “entity instance”
  - o an “instance” is basically a copy of whatever we defined the xor\_gate/and\_gate to be
- the “port map” connects signals in our entity to ports on the instance
  - o  $x \Rightarrow y$  indicates that port x on the instance, y is a signal in the entity we’re defining