

Introduction to Computer Design

SFU, Harbour Centre, Spring 2007

Lecture 9: Feb. 6, 2007


- Programmable Logic Devices (PLDs)
 - Read Only Memory (ROM)
 - Programmable Array Logic (PAL)
 - Programmable Logic Array (PLA)
- Implementing Boolean function using PLDs
- Wired-AND and Wired-OR buses

What does "Programmable" Logic Mean?

- Programming = specifying the interconnections between gates, usually within "arrays" of OR and AND gates.


- Programming Technologies:

- Fuse

 

Every input is connected through a "fuse" to the gate
By "blowing" the fuses connecting a and d we implement bc .*

Notation:

 

* We assume a disconnected input signal carries:

- "1" for an AND gate
- "0" for an OR gate

Review: Chip Design Styles

- Full custom - the entire design of the chip down to the smallest detail of the layout is performed
 - Expensive
 - Justifiable only for dense, fast chips with high sales volume
- Standard cell - blocks have been design ahead of time or as part of previous designs
 - Intermediate cost
 - Less density and speed compared to full custom
- **Gate array** - regular patterns of gate transistors that can be used in many designs built into chip - only the interconnections between gates are specific to a design
 - Lowest cost
 - Less density compared to full custom and standard cell

Logic and Computer Design Fundamentals
PowerPoint Slides
© 2004 Pearson Education, Inc.

What does "Programmable" Logic Mean? (cont')

- Other programming technologies:
 - Antifuse
 - Mask programming
 - Single bit storage element
- Characterization of programming technologies:
 - Permanent - once set cannot be changed
 - Reprogrammable
 - Volatile - programming lost once electric power is off
 - Non-volatile
 - Erasable
 - Electrically erasable
 - Flash (as in Flash Memory)

Why Programmable Logic?


- **Facts:**
 - It is most economical to produce an IC in large volumes
 - Many designs required only small volumes of ICs
- **Need an IC that can be:**
 - Produced in large volumes
 - Handle many designs required in small volumes
- **A programmable logic part can be:**
 - made in large volumes
 - programmed to implement large numbers of different low-volume designs

Programmable Logic - Additional Advantages

- Many programmable logic devices are *field-programmable*, i. e., can be programmed outside of the manufacturing environment
- Most programmable logic devices are *erasable* and *reprogrammable*.
 - Allows “updating” a device or correction of errors
 - Allows reuse the device for a different design - the ultimate in re-usability!
 - Ideal for course laboratories
- Programmable logic devices can be used to prototype design that will be implemented for sale in regular ICs.
 - Complete Intel Pentium designs were actually prototype with specialized systems based on large numbers of VLSI programmable devices!

Types of PLDs

General structure of a PLD:

 

• Types of PLDs:

Device	And-array	Or-array
ROM	Fixed	Programmable
PAL	Programmable	Fixed
PLA	Programmable	Programmable

Read Only Memory


- Read Only Memories (ROM) or Programmable Read Only Memories (PROM) have:
 - N input lines,
 - M output lines, and
 - 2^N decoded minterms.
- Fixed AND array with 2^N outputs implementing all N -literal minterms.
- Programmable OR Array with M outputs lines to form up to M sum of minterm expressions.
- A program for a ROM or PROM is simply a multiple-output truth table
 - If a 1 entry, a connection is made to the corresponding minterm for the corresponding output
 - If a 0, no connection is made
- Can be viewed as a *memory* with the inputs as *addresses of data* (output values), hence ROM or PROM names!

Read Only Memory (cont')

- ROM components can be further classified:
 - ROM:** programmed during manufacture and cannot be changed.
 - Programmable ROM (**PROM**): can be programmed once by the user and cannot reprogrammed afterwards.
 - Erasing PROM (**EPROM**): reprogrammable. Its initial condition can be restored by exposure to ultraviolet light, or by connecting it to high voltage (Electrically Erasable PROM, **EEPROM** or **E²PROM**).
- Writing and erasing EPROMs is much slower than reading.


Read Only Memory Example

 - Example: A 8 X 4 ROM (N = 3 input lines, M= 4 output lines)
- The fixed "AND" array is a "decoder" with 3 inputs and 8 outputs implementing minterms.
- The programmable "OR" array uses a single line to represent all inputs to an OR gate. An "X" in the array corresponds to attaching the minterm to the OR
- Read Example: For input (A₂,A₁,A₀) = 011, output is (F₃,F₂,F₁,F₀) = 0011.
- What are functions F₃, F₂, F₁ and F₀ in terms of (A₂, A₁, A₀)?



Programmable Logic Array (PAL)

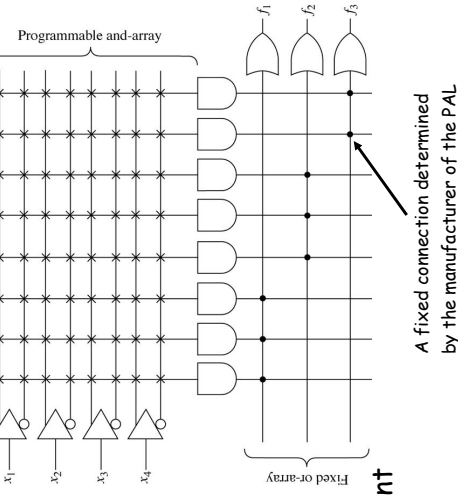- PAL has a programmable AND-array and fixed OR-array




- Example:
 - 4 inputs
 - 3 outputs
 - 8 product terms
 - at most 4 literals
 - 3 sums:
 - 2 of 3 product terms
 - 1 of 2 product terms
- Use this PAL to implement
 - $f_1(x,y,z) = \sum_m(1,2,4,5,7)$
 - $f_2(x,y,z) = \sum_m(0,1,3,5,7)$

Example: Programmable Array Logic

$$f_1(x,y,z) = \sum_m(1,2,4,5,7)$$

$$f_2(x,y,z) = \sum_m(0,1,3,5,7)$$

 

$$f_1(x,y,z) = x\bar{y} + xz + \bar{y}z + x\bar{y}z$$

$$f_2(x,y,z) = z + \bar{x}z$$

- Since in a straight-forward way the PAL can implement sums of at most three product terms, we write:

$$f_1 = f_3 + \bar{y}z + x\bar{y}z$$

$$f_2 = z + \bar{x}z$$


$$f_3 = x\bar{y} + xz$$

Example: Programmable Array Logic (cont')

$$f_1 = f_3 + \bar{y}z + \bar{x}y\bar{z}$$

$$f_2 = z + \bar{x}\bar{z}$$


$$f_3 = x\bar{y} + xz$$

 

- Using a ROM would require implementing all the minterms
- PAL does not guarantee all possible Boolean functions can be implemented.

Programmable Logic Array Example

 
- What are the equations for F_1 and F_2 ?
- Could the PLA implement the functions without the XOR gates?



- 3-input, 3-output PLA with 4 product terms

Programmable Logic Array (PLA)

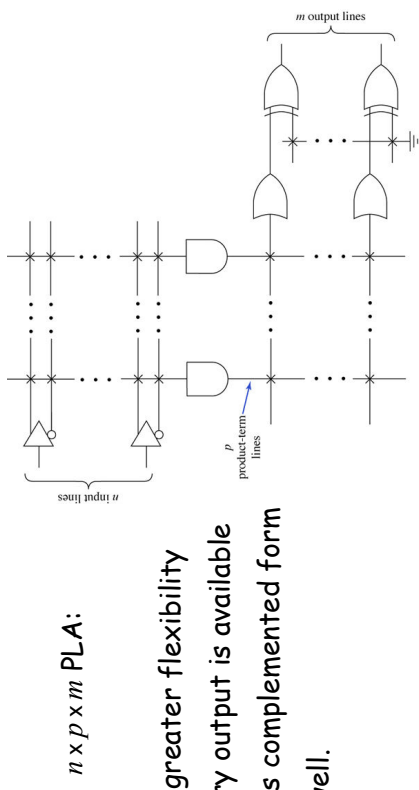- In PLA both the AND-array and OR-array are programmable



$n \times p \times m$ PLA:

- For greater flexibility every output is available in its complemented form as well.

Programmable Logic Array


- The set of functions to be implemented must fit the available number of product terms
- The number of literals per term is less important in fitting
- Since output inversion is available, terms can implement either a function or its complement
- For small circuits, K-maps can be used to visualize product term sharing and use of complements
- For larger circuits, software is used to do the optimization including use of complemented functions

Example

- Implement the following functions using a $3 \times 4 \times 2$ PLA:


$$F_1(A,B,C) = \sum_m(0,1,2,4)$$

$$F_2(A,B,C) = \sum_m(0,5,6,7)$$

 

$$F_1 = \overline{A}B + \overline{A}C + \overline{B}C$$
 
$$F_1 = \overline{A}B + \overline{A}C + \overline{B}C$$



$$F_2 = AB + AC + \overline{A}\overline{B}\overline{C}$$


$$F_2 = \overline{A}C + \overline{A}B + \overline{A}C$$

- Specify the PLA connections by a PLA table:

Product term	Inputs			Outputs	
	A	B	C	F ₁	F ₂
1	1	1	-	1	1
2	1	-	1	1	1
3	-	1	1	1	1
4	0	0	0	-	1

- "1" = connection with variable
- "0" = connection with complement
- "-" = no connection
- T/C = which form of output

Programmable Logic Array Example

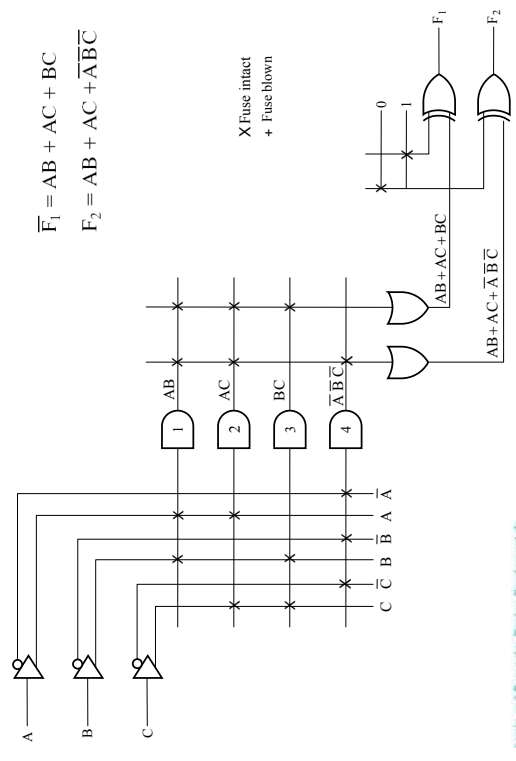


Logic and Computer Design Fundamentals
PowerPoint Slides
© 2004 Pearson Education, Inc.

Wired-AND and Wired-OR Buses

- Implementing the medium-scale integrated (MSI) circuits we mentioned (decoders, encoders, multiplexers, LPDs) require ANDing and ORing of many signals.
- AND/OR gates with large fan-in consume more power, are more expensive, and might not be available.
- Solutions:
 - "Tree" of gates.
 - Wired-AND and Wired-OR buses.

Implementing Logic Gates using Switches

 - The technological implementation of logic gates is done using transistors that implement switches.
- A switch is connected to 3 wires:
 - A control signal (C)
 - 2 wire endpoints that can be connected by the switch (A,B)
- We define two types of switches:



P switch

C	Switch status
0	disconnected
1	connected

N switch


C	Switch status
0	disconnected
1	connected

Implementing Logic Gates using Switches (cont')

- Examples


- Building an inverter

$$B = \bar{A}$$

 

- Building a NAND gate


$$Z = \text{NAND}(A, B)$$

 


3-State Inverter

- We define a new gate using switches:

 - Enable=1: Inverter
- Enable=0: No logic value assigned to B! In this case we say the value of B is Hi-Z.




The gate is called 3-state inverter

 


3-State Bus

 - It is possible to connected several outputs of 3-state gates, as long as only one of them writes to the common output (=BUS).
- To guarantee this we can use a decoder.




 - This component (BUS+decoder) is actually a 4-to-1 multiplexer




Pull-Down and Pull-Up Gates

 - To remove the need for a decoder we define 2 new gates based on the NOT gate:



Wired-AND BUS

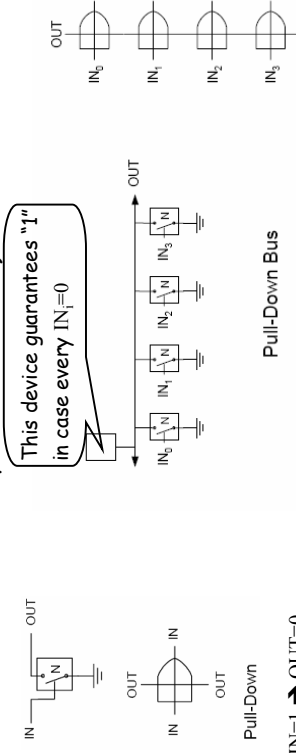- Connecting several pull-down gates to a common output results in a **Wired-AND Bus** (if at least one output is "1" then the value on the bus is "0", otherwise - "1").



Pull-Down

IN=1 → OUT=0


IN=0 → OUT=Hi-Z

- The implemented function is NOR (or AND of the complements)

$NOR(IN_0, IN_1, \dots, IN_k) = \overline{AND(\overline{IN_0}, \overline{IN_1}, \dots, \overline{IN_k})}$

Wired-OR BUS

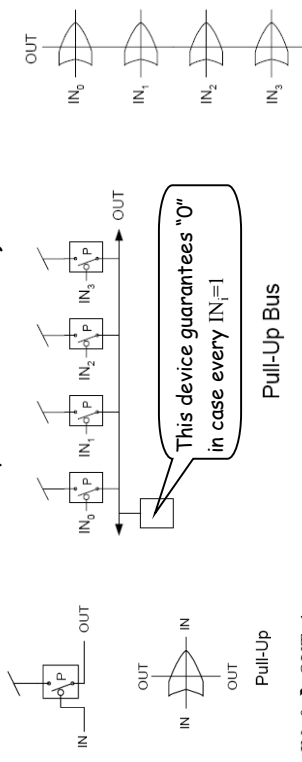- Connecting several pull-up gates to a common output results in a **Wired-OR Bus** (if at least one output is "0" then the value on the bus is "1", otherwise - "0").



Pull-Up

IN=0 → OUT=1

IN=1 → OUT=Hi-Z

- The implemented function is NAND (or OR of the complements)

$NAND(IN_0, IN_1, \dots, IN_k) = \overline{OR(\overline{IN_0}, \overline{IN_1}, \dots, \overline{IN_k})}$