 


May 14
Lecture #5

Full adder

- structural description



architecture struct of full_adder is

```
    signal Sout1, Cout1, Cout2: std_logic;
begin
    HA1: entity work.half_adder
        port map(
            x => x,
            y => y,
            s => Sout1,
            c => Cout1);
    HA2: entity work.half_adder
        port map(
            x => Sout1
            y => Z
            s => S
            c Cout2);
    OR1: entity work.or_gate
        portmap (
            a => Cout2.
            b => Cout1,
            c => C);
end struct;
```

- this circuit needs some connection to hook the entity together
 - o signals Cout1, Cout2, Sout1 are defined as std_logic
 - o signals and parts are treated similarly
- One of the reasons to describe circuits in VHDL is simulation
 - o we need to connect the ports of a circuit, so we can see it work
 - o this is done w/ a “test bench”

- the test bench is self-contained (no ports)
- we simulate the test bench
- our test bench will be called “tb” and have no ports:

```
entity tb is
end tb;
architecture behave of tb is
    signal X, Y, Z, S, C: std_logic;
begin
    TEST: process
    begin
        x <= '0';
        y <= '0';
        z <= '0';
        wait for 100 ns;
        x <= '1';
        wait for 50 ns;
        y <= '1';
        wait for 50 ns;
        z <= '1';
        wait for 50 ns;
    end process
    UUT: entity work.full_adder (struct)
        port map (x=>x y=>y, z=>z, s=>s, c=>c);
end behave;
```

- process always run as often as possible
 - w/ a dependency list
 - process (a, b, c)
 - is only allowed to start when the signals change
- other wise, it starts again immediately
- so, ever process should have either r a dependency list or waits
- when instantiating, we can specify the implementation:


```
entity work.thing (behave)
```

wait:

- makes the process pause
- three versions
 1. wait for <time>;
 - pause for the given time (simulation)
 2. wait until <condition>;
 - pause until the condition is true
 - ie. wait until c='1';
 3. wait on <signal list>
 - wait until one of the signals change
 - eg.

| | |
|-------------------------------------|--|
| <pre>process (a, b) </pre> | <pre>process wait on a, b; </pre> |
|-------------------------------------|--|

end process;

end process;

Latches in VHDL

- SR-Latch



```
entity sr_latch is
  port (
    sr: in std_logic;
    q, q_b: out std_logic);
end sr_latch;
architectural behave of sr_latch is
begin
  sr_process: process (s,r)
  begin
    if s = "1" then
      q <= "1";
      q_b <= "0";
    elsif r = "1" then
      q <= "0";
      q_b <= "1";
    end if
  end process;
end behave;
```