

state	G	READY	N	M	P	C	A	B
IDLE	0	1	1011	1110				
IKDLE	1	1						
IDLE	0	0			11	0	0000	0000
MUL0								
SHIFT				111	10	0	0000	0000
MUL0						0	1011	
SHIFT				11	01	0	0101	1000
MUL0						0	1011	
SHIFT				1	00	0	1000	0100
MUL0						1	0000	
SHIFT					11	0	1001	1010
IDLE	1							

1 0 1 1
 1 1 1 0
 0 0 0 0
 1 0 1 1
 1 0 1 1
 1 0 1 1

1 0 0 1 1 0 1 0

Control Circuit Design

ASM can be easily turned into a control circuit. We need inputs & outputs for the state & control signals inputs:

G

M_0

Z: value of P = 0

Outputs:

Int: trigger A $\leftarrow 0$ B $\leftarrow 0$

Load: do $a \leftarrow A + N$

Shift_dec: do $C \parallel A \parallel B \dots$

Now we need to design circuit that implements the behavior of the ASM

Two ways to do this

One Flip Flop per State

- Each part of the ASM turns into circuit as follows

A signal in the circuit will track our position in the ASM

1= "I'm here"

The operations corresponding to control outputs

Conditions correspond to states signals

Example : the slower multiplier

Input C: $I > 0$

Start

Output: init: $I \leftarrow M$, $P \leftarrow O$

Add: $P \leftarrow P + N$, $I \leftarrow I - 1$