

The Datapath

- The datapath consists of the register file and function unit
- The register file has some registers, each with a fixed number of bits
- The function unit consists of circuitry to do calculations
 - o Eg adder, shifter, multiplier etc
 - o One data out for the result

$N = \#$ of bits per word

$K =$ bits required to select a register. Number of register $\leq 2^k$

- These can be connected to form a datapath:

drawing

The ALU

- The arithmetic/logic unit part of the function unit
- Our ALU will have 3 select lines:
 - o S_2 : do a logic (1) or arithmetic (0) operation
 - o S_1, S_2 : specify the operation

Arithmetic

- The arithmetic circuit is based around an a-bit adder
 - o Some extra logic around it will make a very flexible circuit:

drawing

The B input logic will produce these outputs depending on S_1, S_0 :

S_1	S_0	Out
-------	-------	-----

0	1	all 0's
0	0	B
1	1	!B
1	0	all 1's

This can be implemented with n of these:

drawing

- The output of the ALU will be $A + Y + C_{in}$
- That allows these operations:

S_1	S_0	C_{in}	Y	Output
0	0	0	zeros	A transfer
0	0	1	zeros	A +1 Increment
0	1	0	B	A+B add
0	1	1	B	A+B+1 add, inc
1	0	0	!B	A + !B add complement
1	0	1	!B	A+!B +1 A-B subtract
1	1	0	ones	A-1 decrement
1	1	1	ones	a-1+1=A transfer

Bu using the correct combination of these select signals (S_1, S_0, S_2) the ALU can do any of these operations