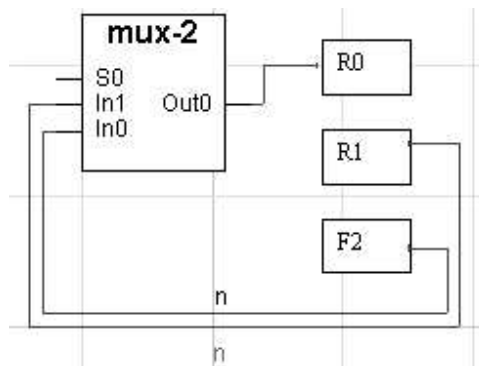


Register Transfers

June 9, 2003


- We need to be able to take data from any register(s), do some calculations and write back to a register
- There are a few ways to do this
 - o We will only worry about register transfer ($RG \leftarrow R0$)
 - o No calculations
- Multiplexer based transfer
 - o Connect a multiplexer :
 - Inputs: output from every register
 - Output: to a register input



- Works if there are a few registers—bad if there are a lot
 - o 32 register: 32 31 to 1 multiplexers and a lot of connections

Bus Based transfer

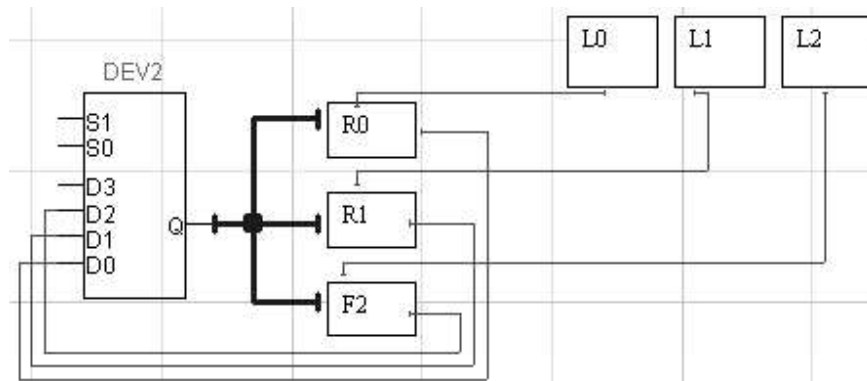- too many multiplexers would mean a large (thus costly) circuit
- we could use a single input line for all registers
 - o a “bus”
 - o (any shared single is a “bus”)
- the multiplexer will be connected to every input:



Eg. To do $R0 \leftarrow R2$


- select input 2 ($S_1 = 1, S_0 = 0$)
- set $L0 \leftarrow 1$;

Eg. $R0 \leftarrow R2, R1 \leftarrow R2$


- select input 2 ($S_1 = 1, S_0 = 0$)
- set $L0 \leftarrow 1, L1 \leftarrow 1$
- $R1 \leftarrow R0, R0 \leftarrow R1$
 - o Can't o
 - o Could have done with the multiplexer solution

The State Bus

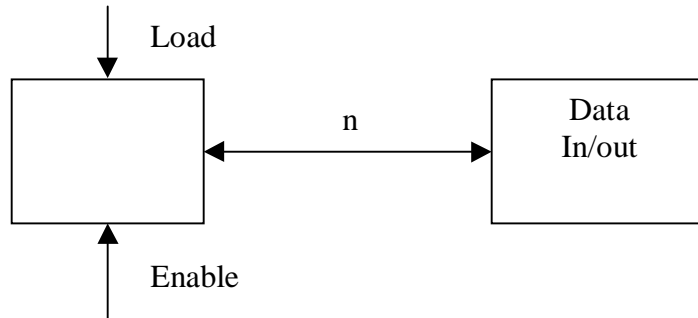- We can use three-state buffer to get rid of the multiplexers all together
 - o We will use a single bus for both input & output
 - o A "bidirectional bus"
- We need a register with bidirectional input/output



Tri State Buffer

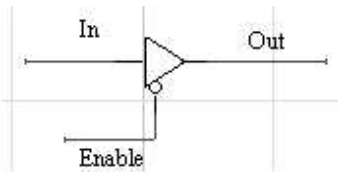

- When En is 1, it behaves like a buffer (output the input signal)
- When En is 0, don't allow any current in either direction


In	En	Out
0	1	0
1	1	1
0	0	Hi-Z
1	0	Hi-Z

Hi-Z = high impedance


- No current allow past
- In VHDL: 'Z'

- Building a bidirectional register:


- Using a standard register:

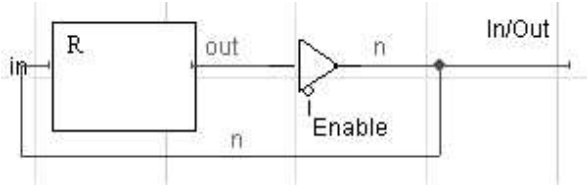

Standard Symbol

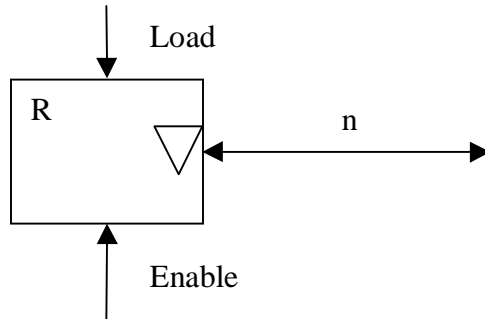

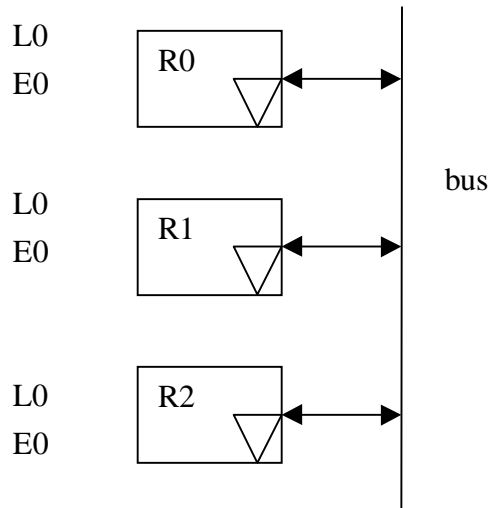We can now connect some bi-di-register on a bus:



At most of the enable signal can be 1 at a time

Eg. To do $R0 \leftarrow R2$

- set $E2=1$, $L0 \leftarrow 1$

Eg. To do $R0 \leftarrow R2$ $R1 \leftarrow R2$

- $E2 = 1$, $L0 = 1$, $L1 = 1$

Using a signal bus for input & output halves the # of connections

- Less circuitry

-