 



Synthesizing VHDL

- The real goal in writing VHDL is to create a (physical) circuit
 - o To do this, a VHDL description must be translated into a circuit diagram
 - o “synthesis
- synthesis tools vary between VHDL implementations
 - o none can synthesis all VHDL
 - o some can do more than others
- the result of synthesis depends on the target
 - o ASIC: application specified integrated circuit
 - A custom chip—target is transistors on silicon
 - o FPGA: field programmable gate array
 - A pre-made chip that can be programmed to do anything.
 - Target: a program for the specific FPGA
- Some VHDL has obvious implementations:

- o `Out<=a and b;`



 - o `Out<= (In0 and (not sel))`
`or (In1 and sel)`
 - A 2 to 1 mux



- Some is less obvious
 - If `sel = '1'` then
`Out <=In1;`
 - Else
`Out <=In0;`
 - End if;

 - If `rising_edge (clock)`
`G <= d;`
 - End if;

- Most implementation should be able to deal with these
- Structural implementations are (obviously) easy to turn into circuits
 - o Good for pre-existing components or getting around limitations in synthesis tools
 - o Also for hand-optimizing
- Only these std_logic values have meaning in synthesis: '0', '1', 'Z',
 - o E.g.
if sel = '0' then
 out <= In0,
elseif sel = '1' then
 out <= In1;
else
 out <= '-';
end if;
- The “after” quantifier can't be synthesized
 - o The delay comes from the implementation.
 - o It's there for the simulation
 - To make it look more like the real circuit
 - Assuming delays are guessed well.