

Digital Logic - Combinational



Agenda

- Combinational Logic
 - Combinational Logic Gates
 - Truth Tables
 - Boolean Algebra
 - Circuit Simplification

Roadmap

C:

```

car *c = malloc(sizeof(car));
c->miles = 100;
c->gals = 17;
float mpg = get_mpg(c);
free(c);

```

Java:

```

Car c = new Car();
c.setMiles(100);
c.setGals(17);
float mpg =
    c.getMPG();

```

Assembly
language:

```

get_mpg(car*):
    lw    a5,0(a0)
    lw    a4,4(a0)
    divw  a5,a5,a4
    fcvt.s.w    fa0,a5
    ret

```



Machine
code:

```

0111010000011000
100011010000010000000010
1000100111000010
110000011111101000011111

```

Computer
system:

  

Memory & data
Arrays & structs
Integers & floats
RISC V assembly
Procedures & stacks
Executables
Memory & caches
Processor Pipeline
Performance
Parallelism

OS:



Why is this important?

- Why study hardware design?
 - Background for other more in-depth classes
 - Only course in CMPT that deals with hardware
 - We need some digital systems knowledge to build our own processor

Why is this important?

- We need some digital systems knowledge to build our own processor
- Why build our own processor?
 - Because we believe computer scientists should have an answer to the question “How does a computer work?”
 - So you can understand how code is actually executed on a computer

Why is this important?

- So you can understand how code is actually executed on a computer
- Why do we care about how code executes?
 - Reliability
 - Performance
 - Security

Hardware Design

Why study hardware design and processors and computers if you only care about high-level software?

Example of the power of layered abstractions

- Transistors -> Combinational Logic
- Combinational Logic -> Sequential Logic
- Sequential Logic -> Processors
- Processors -> Machine Language
- Machine Language -> Assembly
- Assembly -> High-level Programming Languages
- High-level Programming Languages -> Word, Minecraft, Twitter

At each step we can “abstract away” the lower steps and (mostly) forget they exist

Synchronous Digital Systems (SDS)

Hardware of a processor, such as a RISC-V processor, is an example of a Synchronous Digital System

Synchronous:


- All operations coordinated by a central clock
 - “Heartbeat” of the system! (processor frequency)

Digital:

- Represent all values with two discrete values
- Electrical signals are treated as 1's and 0's
 - 1 and 0 are complements of each other
- High/Low voltage for True/False, 1/0

Moore's Law – The number of transistors on integrated circuit chips (1971-2018)

 Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important as other aspects of technological progress – such as processing speed or the price of electronic products – are linked to Moore's law.



Data source: Wikipedia (https://en.wikipedia.org/wiki/Transistor_count)
 The data visualization is available at [OurWorldinData.org](https://www.ourworldindata.org). There you find more visualizations and research on this topic.

Licensed under CC-BY-SA by the author Max Roser.

Historical Trend

Trend:

- Hardware gets more powerful every year.
 - (Really due to hard work of thousands of engineers)

Therefore:

- Software gets more resources and faster compute!
 - (And has to keep up with ever-changing hardware)

Agenda

- **Combinational Logic**
 - **Combinational Logic Gates**
 - Truth Tables
 - Boolean Algebra
 - Circuit Simplification


Type of Circuits

- *Digital Systems* consist of two basic types of circuits:
 - Combinational Logic (CL)
 - Output is a function of the inputs only, not the history of its execution
 - e.g. circuits to add A, B (ALUs)
 - Sequential Logic (SL)
 - Circuits that “remember” or store information
 - a.k.a. “State Elements”
 - e.g. memory and registers (Registers)

Logic Gates (1/2)

- Special names and symbols:

NOT

 

a	c
0	1
1	0

AND



a	b	c
0	0	0
0	1	0
1	0	0
1	1	1

OR



a	b	c
0	0	0
0	1	1
1	0	1
1	1	1

Logic Gates (2/2)

Inverted versions are easier to implement in CMOS

NAND



a	b	c
0	0	1
0	1	1
1	0	1
1	1	0

NOR




a	b	c
0	0	1
0	1	0
1	0	0
1	1	0

XOR



a	b	c
0	0	0
0	1	1
1	0	1
1	1	0

Combining Multiple Logic Gates

 

(NOT(A AND B)) AND (A OR (NOT B AND C))

Agenda

- **Combinational Logic**
 - Combinational Logic Gates
 - **Truth Tables**
 - Boolean Algebra
 - Circuit Simplification


Representations of Combinational Logic

- ✓ Text Description
 - ✓ Circuit Diagram
 - Transistors and wires
 - Logic Gates
 - ✓ Truth Table
 - ✓ Boolean Expression
- ✓ All are equivalent*

Truth Tables

- Table that relates the inputs to a combinational logic circuit to its output
 - Output *only* depends on current inputs
 - Use abstraction of 0/1 instead of high/low V
 - Shows output for *every* possible combination of inputs
- How big?
 - 0 or 1 for each of N inputs, so 2^N rows

General Form

 


A	B	C	Y	
0	0	0	$F(0,0,0)$	0
0	0	1	$F(0,0,1)$	1
0	1	0	$F(0,1,0)$	0
0	1	1	$F(0,1,1)$	0
1	0	0	$F(1,0,0)$	0
1	0	1	$F(1,0,1)$	1
1	1	0	$F(1,1,0)$	1
1	1	1	$F(1,1,1)$	0

If N inputs, how many distinct functions F do we have?

Function maps each row to 0 or 1,
so **2^N possible functions**

Multiple Outputs

 

- For 3 outputs, just three indep. functions:
 $X(A,B,C,D)$, $Y(A,B,C,D)$, and $Z(A,B,C,D)$
 - Can show functions in separate columns without adding any rows!

Question: Convert the following statements into a Truth Table for: $(x \text{ XOR } y) \text{ OR } (\text{NOT } z)$

X	Y	Z	(A)	(B)	(C)	(D)
0	0	0	1	1	1	1
0	0	1	0	0	0	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	0	1	1	1
1	0	1	1	1	0	1
1	1	0	1	1	1	0
1	1	1	1	0	1	1

Question: Convert the following statements into a Truth Table for: $(x \text{ XOR } y) \text{ OR } (\text{NOT } z)$


X	Y	Z	(A)	(B)	(C)	(D)
0	0	0	1	1	1	1
0	0	1	0	0	0	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	0	1	1	1
1	0	1	1	1	0	1
1	1	0	1	1	1	0
1	1	1	1	0	1	1

More Complicated Truth Tables

3-Input Majority

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

2-bit Adder

 

How many rows?

A		B		C		
a_1	a_0	b_1	b_0	c_2	c_1	c_0
			.			
			.			
			.			

Agenda

- **Combinational Logic**
 - Combinational Logic Gates
 - Truth Tables
 - **Boolean Algebra**
 - Circuit Simplification

My Hand Hurts...

- Truth tables are huge
 - Write out EVERY combination of inputs and outputs (thorough, but inefficient)
 - Finding a particular combination of inputs involves scanning a large portion of the table
- There must be a shorter way to represent combinational logic
 - Boolean Algebra to the rescue!

Boolean Algebra

- Represent inputs and outputs as variables
 - Each variable can only take on the value 0 or 1
 - Overbar or $\bar{}$ is NOT: “logical complement”
 - e.g. if A is 0, \bar{A} is 1. If A is 1, then \bar{A} is 0
 - Plus (+) is 2-input OR: “logical sum”
 - Product (\cdot) is 2-input AND: “logical product”
 - All other gates and logical expressions can be built from combinations of these
- $\bar{A}B + A\bar{B} == (\text{NOT}(A \text{ AND } B)) \text{ OR } (A \text{ AND NOT } B)$

← For slides,
will use \bar{A}

Laws of Boolean Algebra

These laws allow us to perform simplification:

$$x \cdot \bar{x} = 0$$

$$x \cdot 0 = 0$$

$$x \cdot 1 = x$$

$$x \cdot x = x$$

$$x \cdot y = y \cdot x$$

$$(xy)z = x(yz)$$

$$x(y + z) = xy + xz$$

$$xy + x = x$$

$$\bar{x}y + x = x + y$$

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

$$x + \bar{x} = 1$$

$$x + 1 = 1$$

$$x + 0 = x$$

$$x + x = x$$

$$x + y = y + x$$

$$(x + y) + z = x + (y + z)$$

$$x + yz = (x + y)(x + z)$$

$$(x + y)x = x$$

$$(\bar{x} + y)x = xy$$

$$\overline{x + y} = \bar{x} \cdot \bar{y}$$

complementarity

laws of 0's and 1's

identities

idempotent law

commutativity

associativity

distribution

uniting theorem

uniting theorem v.2

DeMorgan's Law

Truth Table to Boolean Expression

- Read off of table
 - For 1, write variable name
 - For 0, write complement of variable
- *Sum of Products (SoP)*
 - Take rows with 1's in output column, sum products of inputs

a	b	c
0	0	0
0	1	1
1	0	1
1	1	0

- $c = \neg a b + a \neg b$

We can show that these are equivalent!

- *Product of Sums (PoS)*
 - Take rows with 0's in output column, product the sum of the *complements of the inputs*
 - $c = (a + b) \cdot (\neg a + \neg b)$

Faster Hardware?

- **Recall:** Everything we are dealing with is just an abstraction of transistors and wires
 - Inputs propagating to the outputs are voltage signals passing through transistor networks
 - There is always some *delay* before a CL's output updates to reflect the inputs
- Simpler Boolean expressions \leftrightarrow smaller transistor networks \leftrightarrow smaller circuit delays \leftrightarrow faster hardware

Agenda


- **Muxes**
- Sequential Logic Timing
- Maximum Clock Frequency
- Finite State Machines
- Functional Units
- Summary

Bonus Slides

- Logisim Intro

Data Multiplexor

 - Multiplexor (“MUX”) is a *selector*
 - Place one of multiple inputs onto output (N-to-1)
- Shown below is an n-bit 2-to-1 MUX
 - Input S selects between two inputs of n bits each




This input is passed to output if selector bits match shown value

Represents that this wire has n bits

Implementing a 1-bit 2-to-1 MUX

- Schematic:**

 


- Truth Table:**

s	a	b	c
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- Boolean Algebra:**


$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$

- Circuit Diagram:**

 

1-bit 4-to-1 MUX (1/2)

- **Schematic:**

 


- **Truth Table:** How many rows? 2^6
- **Boolean Expression:**

$$e = \neg s_1 \neg s_0 a + \neg s_1 s_0 b + s_1 \neg s_0 c + s_1 s_0 d$$

1-bit 4-to-1 MUX (2/2)

 - Can we leverage what we've previously built?
 - Alternative hierarchical approach:



Bonus slides (not testable)

Agenda

- **Combinational Logic**
 - Combinational Logic Gates
 - Truth Tables
 - Boolean Algebra
 - **Circuit Simplification**


Manipulating Boolean Algebra

- SoP and PoS expressions can still be long
 - We wanted to have shorter representation than a truth table!
- Boolean algebra follows a set of rules that allow for simplification
 - Goal will be to arrive at the simplest equivalent expression
 - Allows us to build simpler (and faster) hardware

Boolean Algebraic Simplification Example

$$y = ab + a + c$$

Circuit Simplification

 


1) original circuit (Transistors and/or Gates)

$$y = ((ab) + a) + c$$

2) equation derived from original circuit

$$\begin{aligned} &\downarrow \\ &= ab + a + c \\ &\downarrow \\ &= a(b + 1) + c \\ &= a(1) + c \\ &= a + c \end{aligned}$$

3) algebraic simplification

 


4) simplified circuit

Representations of Combinational Logic


- ✓ Text Description
 - ✓ Circuit Diagram
 - Transistors and wires
 - Logic Gates
 - ✓ Truth Table
 - ✓ Boolean Expression
- ✓ All are equivalent*

Converting Combinational Logic

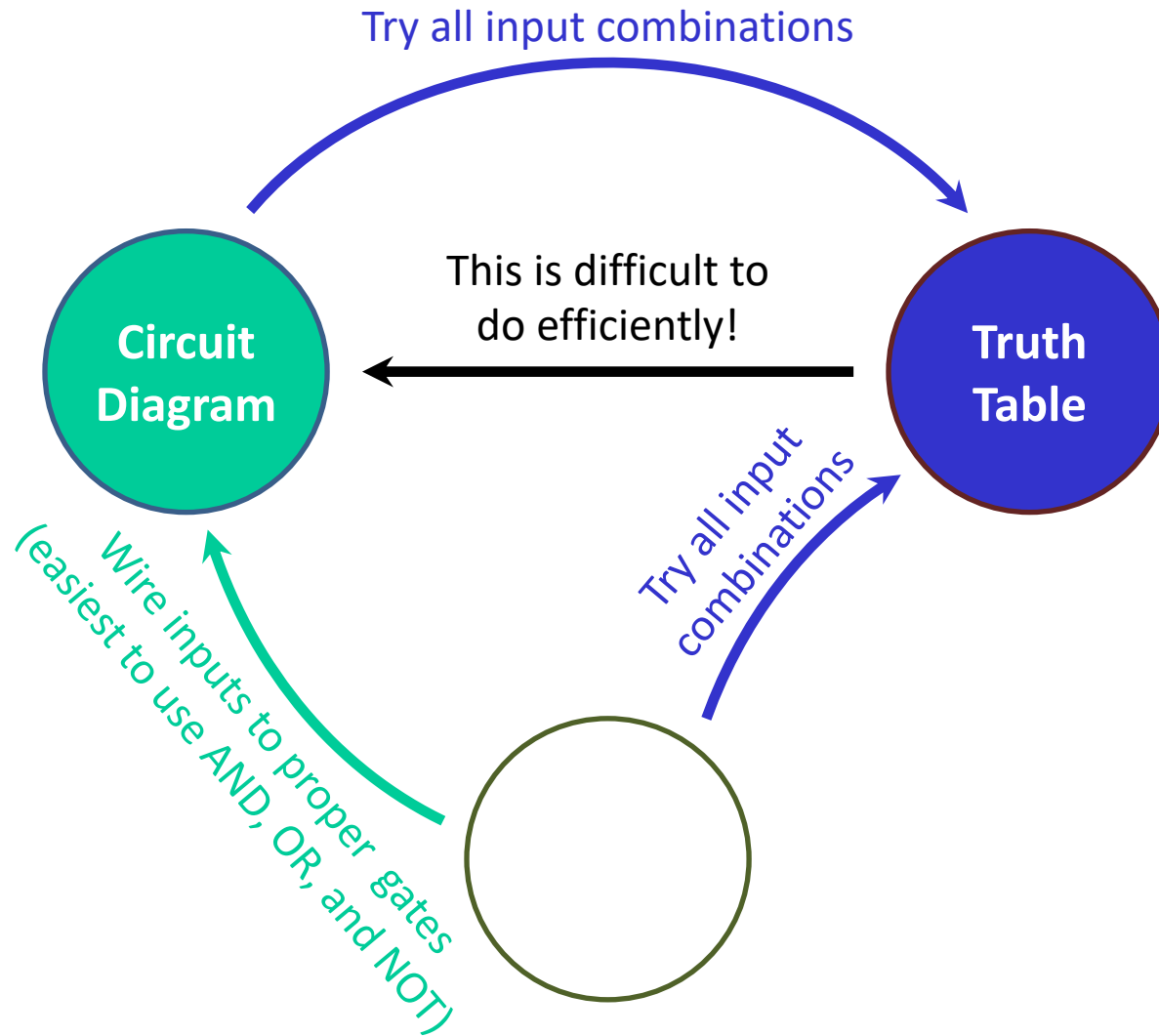

Circuit Simplification Example (1/4)


- Simplify the following circuit:

 

- Options:
 - 1) Test all combinations of the inputs and build the Truth Table, then use SoP or PoS
 - 2) Write out expressions for signals based on gates
 - Will show this method here

Circuit Simplification Example (2/4)

- Simplify the following circuit:

 

- Start from left, propagate signals to the right

Arrive at $D = \neg(AB)(A + \neg BC)$

Circuit Simplification Example (3/4)

- Simplify Expression:

$$D = \neg(AB)(A + \neg BC)$$

$$= (\neg A + \neg B)(A + \neg BC)$$

DeMorgan's

$$= \neg AA + \neg A\neg BC + \neg BA + \neg B\neg BC$$

Distribution

$$= 0 + \neg A\neg BC + \neg BA + \neg B\neg BC$$

Complementarity

$$= \neg A\neg BC + \neg BA + \neg BC$$

Idempotent Law

$$= (\neg A + 1)\neg BC + \neg BA$$

} Which of these
is "simpler"?


Circuit Simplification Example (4/4)

- Draw out final circuit:

$$- D = \underbrace{-BC}_5 + \underbrace{-BA}_3 = \underbrace{-B(A + C)}_3$$

How many gates do we need for each?

- Simplified Circuit:

 

- Reduction from 6 gates to 3!