

Digital Logic - Sequential



Roadmap

C:

```
car *c = malloc(sizeof(car));
c->miles = 100;
c->gals = 17;
float mpg = get_mpg(c);
free(c);
```

Java:

```
Car c = new Car();
c.setMiles(100);
c.setGals(17);
float mpg =
    c.getMPG();
```

Memory & data
Arrays & structs
Integers & floats
RISC V assembly
Procedures & stacks
Executables
Memory & caches
Processor Pipeline
Performance
Parallelism

Assembly
language:

```
get_mpg(car*):
    lw    a5,0(a0)
    lw    a4,4(a0)
    divw  a5,a5,a4
    fcvt.s.w    fa0,a5
    ret
```



Machine
code:

```
0111010000011000
100011010000010000000010
1000100111000010
110000011111101000011111
```

OS:



Computer
system:

  

Agenda

- Muxes
- **Sequential Logic Timing**
- Maximum Clock Frequency
- Finite State Machines
- Functional Units
- Summary

Bonus Slides

- Logisim Intro

Type of Circuits

- *Digital Systems* consist of two basic types of circuits:
 - Combinational Logic (CL)
 - Output is a function of the inputs only, not the history of its execution
 - e.g. circuits to add A, B (ALUs)
 - Sequential Logic (SL)
 - Circuits that “remember” or store information
 - a.k.a. “State Elements”
 - e.g. memory and registers (Registers)

Accumulator Example

An example of why we would need sequential logic




Want: $S=0;$
 for X_1, X_2, X_3 over time...
 $S = S + X_i$

Assume:

- Each X value is applied in succession, one per cycle
- The sum since time 1 (cycle) is present on S


First Try: Does this work?

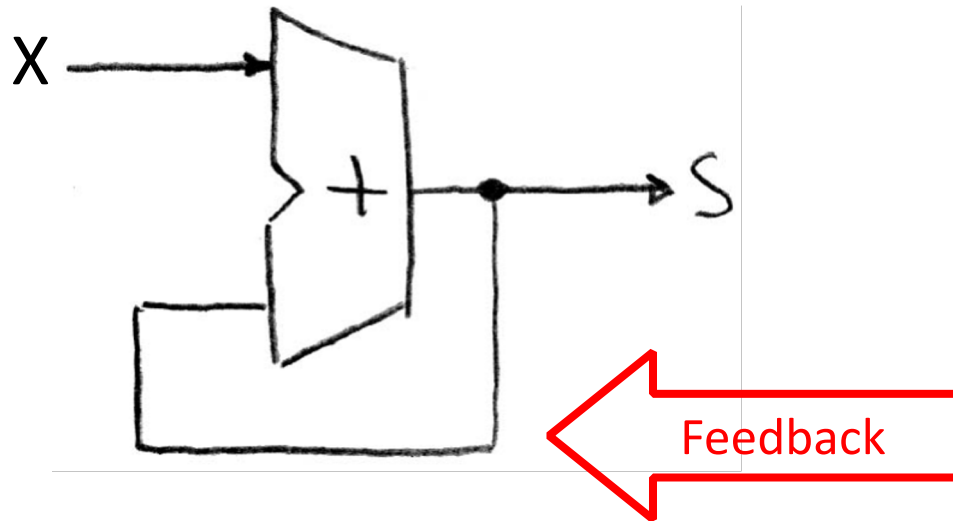

No!

- 1) How to control the next iteration of the 'for' loop?
- 2) How do we say: ' $S=0$ '?

Second Try: How About This?

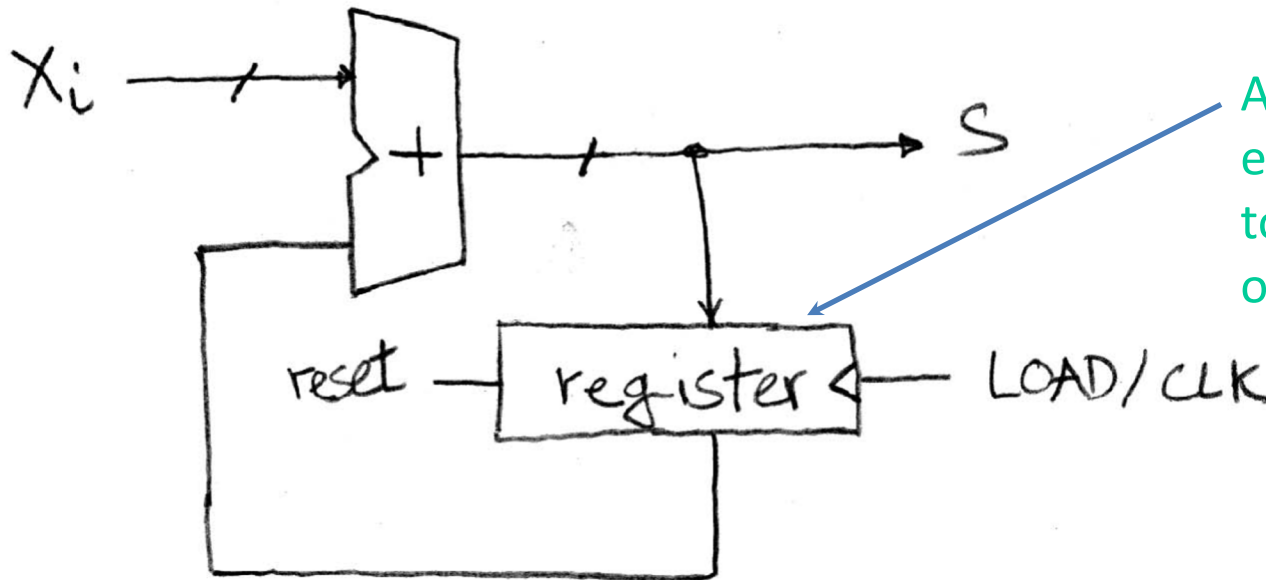

A *Register* is the state element that is used here to hold up the transfer of data to the adder


Uses for State Elements

- Place to store values for some amount of time:
 - Register files (like in RISC-V)
 - Memory (caches and main memory)
- *Help control flow of information between combinational logic blocks*
 - State elements are used to hold up the movement of information at the inputs to combinational logic blocks and allow for orderly passage


Registers

Same as registers in assembly:

- small memory storage locations

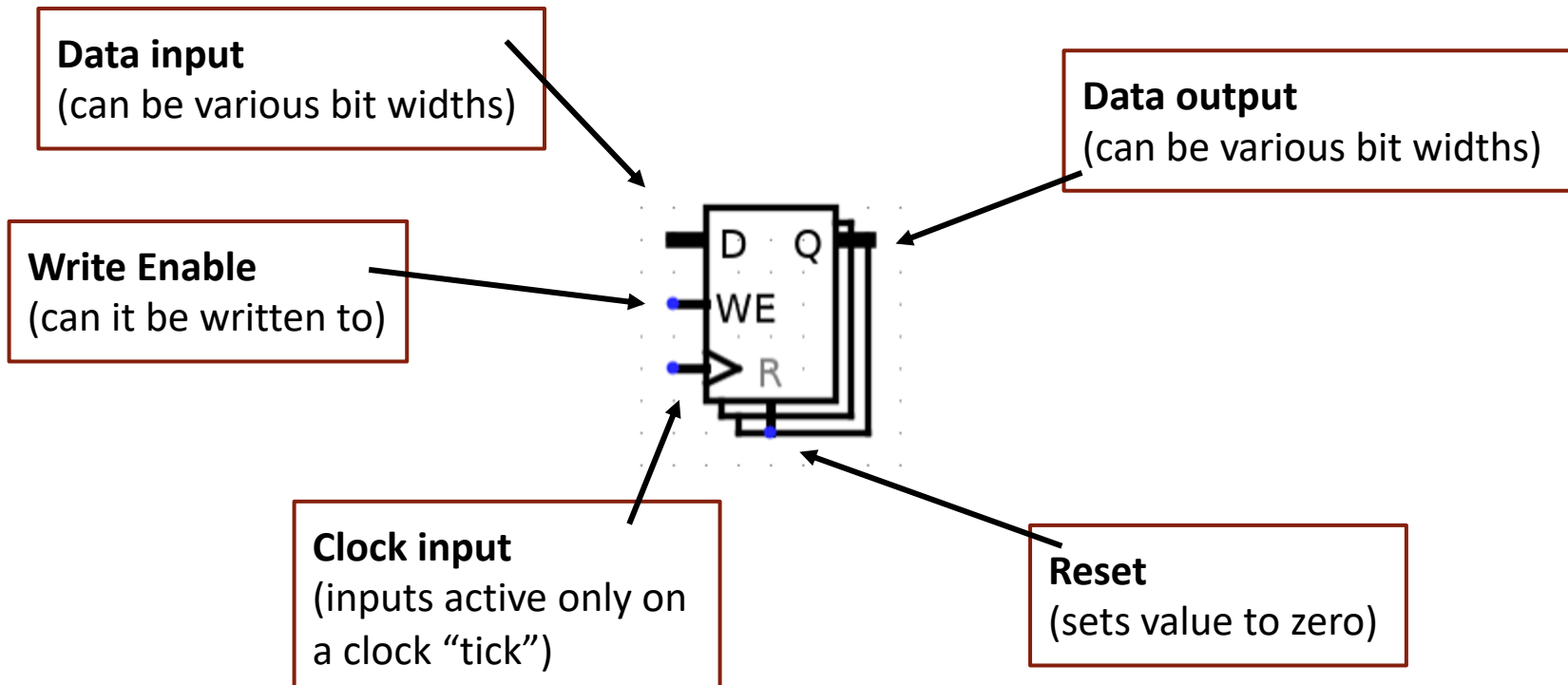


Signals and Waveforms: Clocks

 


- **Signals** transmitted over wires continuously
- Transmission is effectively instantaneous
 - Implies that any wire only contains one value at any given time

Signals and Waveforms

 


Stack
signals
on top
of each
other

 


Dealing with Waveform Diagrams

- Easiest to start with CLK on top
 - Solve signal by signal, from inputs to outputs
 - Can only draw the waveform for a signal if *all* of its input waveforms are drawn
- When does a signal update?
 - A *state element* updates based on CLK triggers
 - A *combinational element* updates ANY time ANY of its inputs changes


Signals and Waveforms: Grouping

 

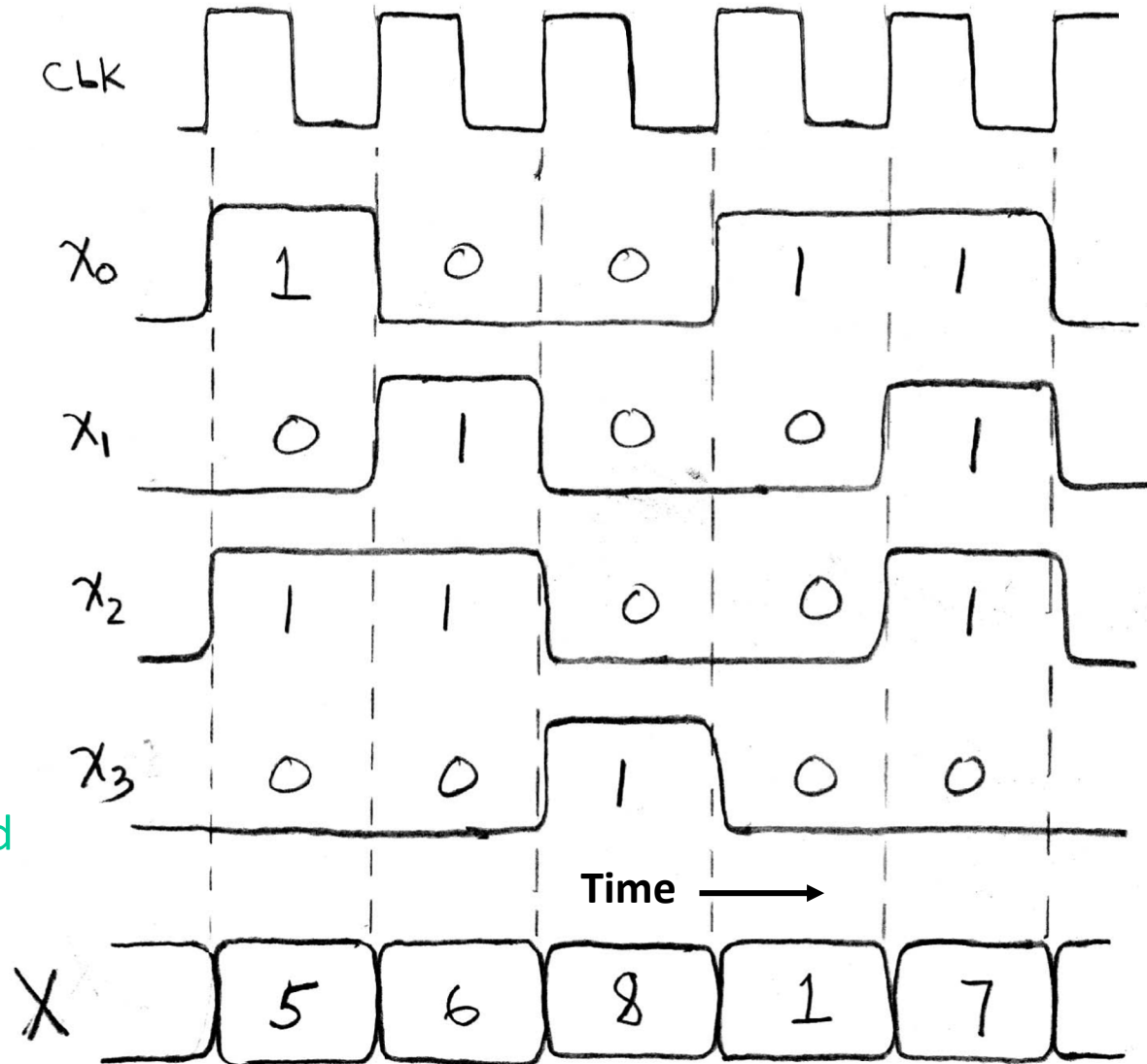
A group of wires when interpreted as a bit field is called a *bus*



Second Try: How About This?

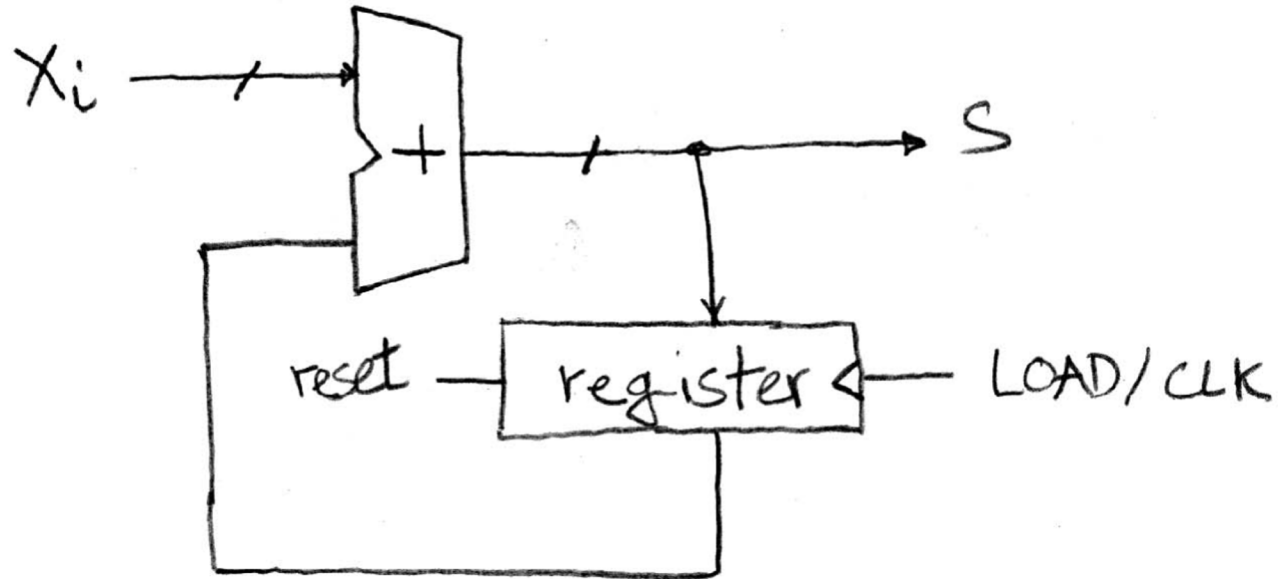

Rough
timing ...

 

Review of Timing Terms

- **Clock:** steady square wave that synchronizes system
- **Register:** several bits of state that samples on rising edge of Clock (positive edge-triggered); also has RESET
- **Setup Time:** when input must be stable *before* Clock trigger
- **Hold Time:** when input must be stable *after* Clock trigger
- **Clock-to-Q Delay:** how long it takes output to change from Clock trigger


Agenda

- Muxes
- Sequential Logic Timing
- **Maximum Clock Frequency**
- Finite State Machines
- Functional Units
- Summary

Bonus Slides

- Logisim Intro

Model for Synchronous Systems

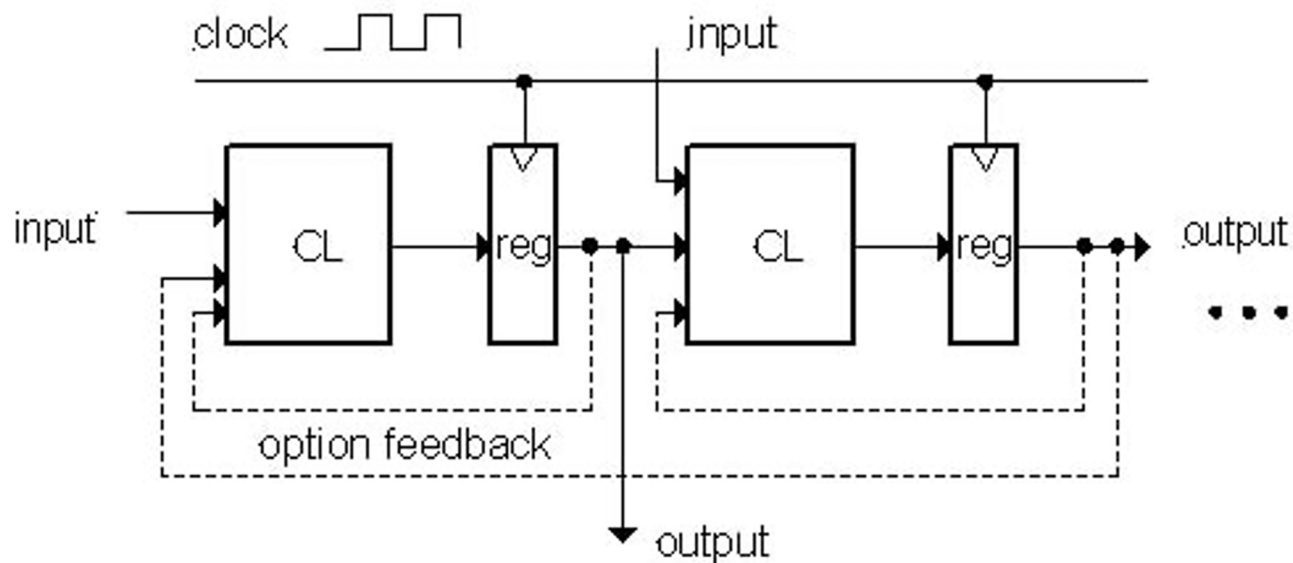


- Combinational logic blocks separated by registers
 - Clock signal connects only to sequential logic elements
 - Feedback is optional depending on application
- How do we ensure proper behavior?
 - How fast can we run our clock?

Maximum Clock Frequency

- What is the max frequency of this circuit?
 - Limited by how much time needed to get correct Next State to Register (t_{setup} constraint)

Assumes Max Delay > Hold Time

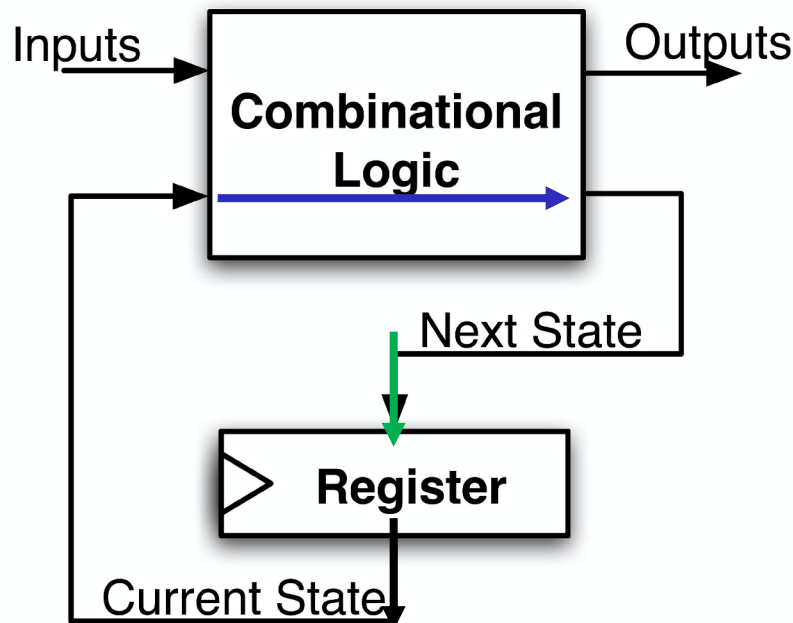


$$\begin{aligned} \text{Max Delay} &= \text{CLK-to-Q Delay} \\ &+ \text{CL Delay} \\ &+ \text{Setup Time} \end{aligned}$$

$$\begin{aligned} \text{Min Period} &= \text{Max Delay} \\ \text{Max Freq} &= 1/\text{Min Period} \end{aligned}$$

The Critical Path

 - The *critical path* is the longest delay between *any* two registers in a circuit
- The clock period must be *longer* than this critical path, or the signal will not propagate properly to that next register




How do we go faster?

Pipelining!


- Split operation into smaller parts and add a register between each one.

Pipelining and Clock Frequency (1/2)


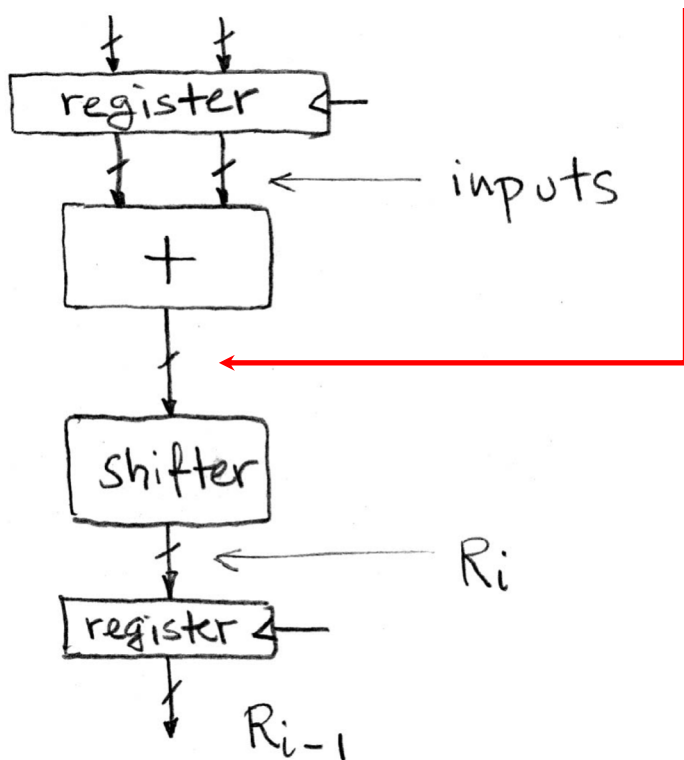
- Clock period limited by propagation delay of adder and shifter
 - Add an extra register to reduce the critical path!



Timing:

 

Pipelining and Clock Frequency (2/2)

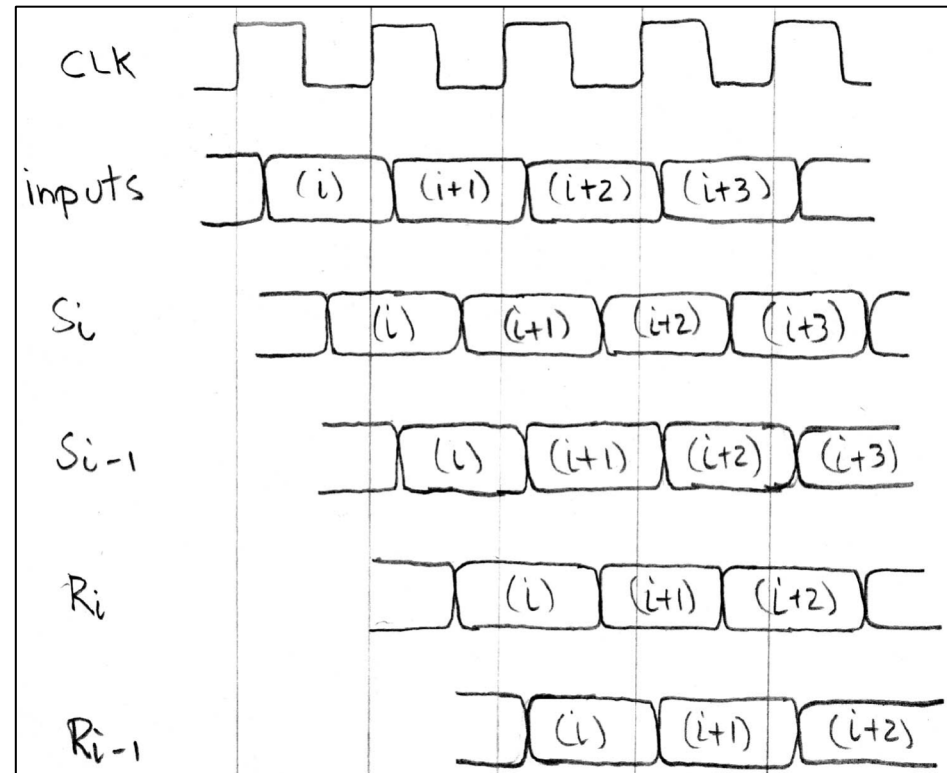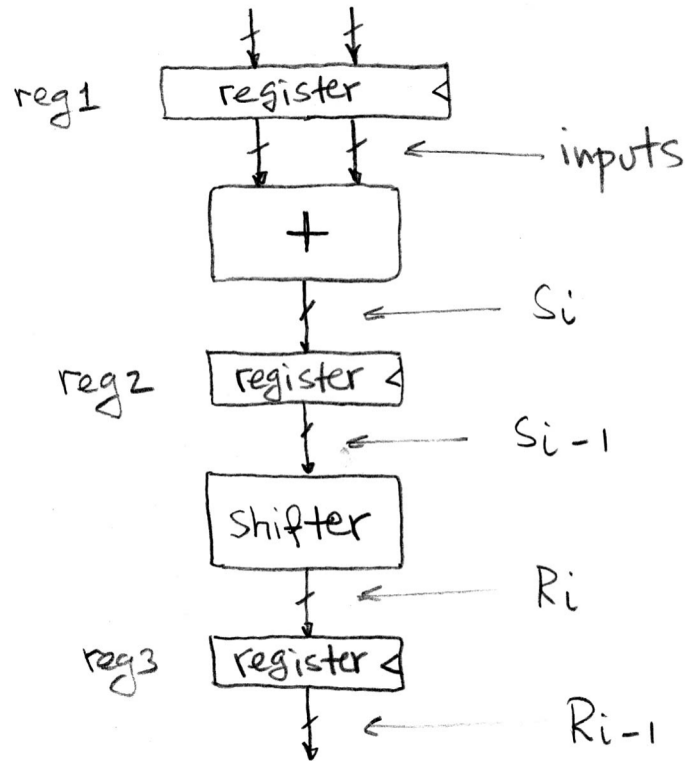

- Reduced critical path \rightarrow allows higher clock freq.
- Extra register \rightarrow extra (shorter) cycle to produce first output


Pipelining Basics

- By adding more registers, break path into shorter “stages”
 - Aim is to reduce critical path
 - Signals take an additional clock cycle to propagate through *each* stage
- New critical path must be calculated
 - Affected by placement of new pipelining registers
 - Faster clock rate → higher throughput (outputs)
 - More stages → higher startup latency
- **Pipelining tends to improve performance**
 - More on this (and application to CPUs) later

Question: Want to run on 1 GHz processor.

$t_{\text{add}} = 100 \text{ ps}$. $t_{\text{mult}} = 200 \text{ ps}$. $t_{\text{setup}} = t_{\text{hold}} = 50 \text{ ps}$.

What is the maximum clock-to-q time?

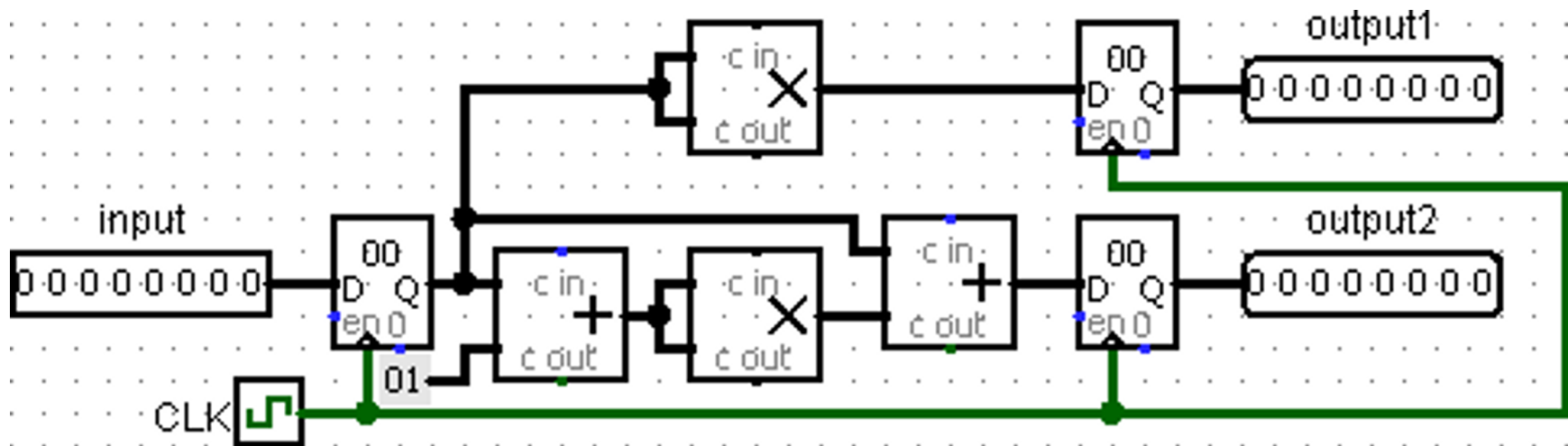

(A) 550 ps

(B) 750 ps


(C) 500 ps

(D) 700 ps

Question: Want to run on 1 GHz processor.

$t_{\text{add}} = 100 \text{ ps}$. $t_{\text{mult}} = 200 \text{ ps}$. $t_{\text{setup}} = t_{\text{hold}} = 50 \text{ ps}$.

What is the maximum clock-to-q time?

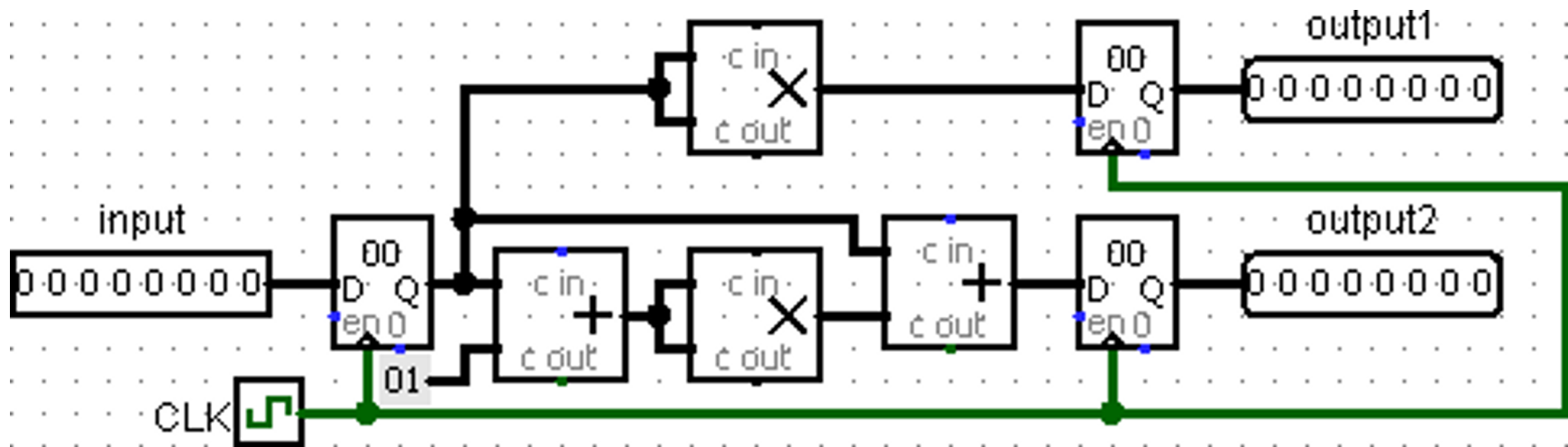

(A) 550 ps

(B) 750 ps

(C) 500 ps

(D) 700 ps

Bottom path is critical path:

clock-to-q + 100 + 200 + 100 + 50 < 1000 ps = 1ns

clock-to-q + 450 < 1000 ps

clock-to-q < 550

Agenda

- Muxes
- Sequential Logic Timing
- Maximum Clock Frequency
- **Functional Units**
- Summary

Bonus Slides

- FSMs

Functional Units (a.k.a. Execution Unit)

- Now that we know sequential logic, we can explore some pieces of a processor!
- Functional Units are a part of the processor that perform operations and calculations based on the running program
 - Arithmetic Logic Unit
 - Floating Point Unit
 - Load/Store Unit
 - and several more...

Invented by *John Von Neumann*


He also invented

- Stored Program Concept
- Mergesort
- Mutually Assured Destruction

Arithmetic Logic Unit (ALU)


- Most processors contain a special logic block called the “Arithmetic Logic Unit” (ALU)
 - We’ll show you an easy one that does ADD, SUB, bitwise AND, and bitwise OR

- **Schematic:**

 

when $S=00$, $R = A + B$
 when $S=01$, $R = A - B$
 when $S=10$, $R = A \text{ AND } B$
 when $S=11$, $R = A \text{ OR } B$

Simple ALU Schematic

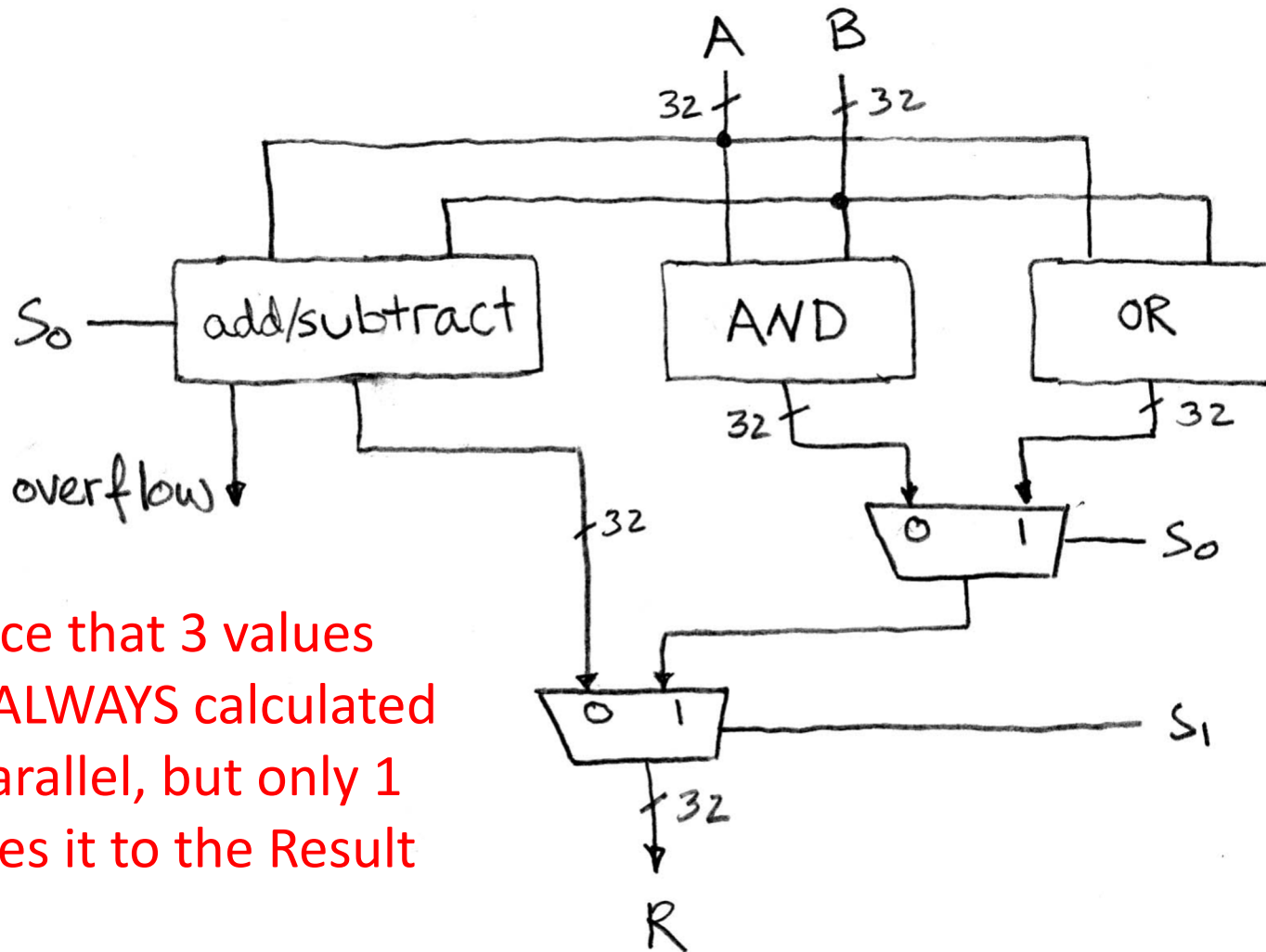

Notice that 3 values
are ALWAYS calculated
in parallel, but only 1
makes it to the Result

Adder/Subtractor Design

- 1) Combinational Logic design we've seen before:
 - write out truth table
 - convert to boolean logic
 - minimize logic
 - then implement

How big might truth table and/or Boolean expression get?

Adder/Subtractor Design

- 2) Break down the problem into smaller pieces that we can cascade or hierarchically layer
 - Let's try this approach instead

Adder/Subtractor: 1-bit LSB Adder

$$\begin{array}{rcccc}
 & a_3 & a_2 & a_1 & a_0 \\
 + & b_3 & b_2 & b_1 & b_0 \\
 \hline
 s_3 & s_2 & s_1 & s_0
 \end{array}$$


Carry-out bit

a_0	b_0	s_0	c_1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 = a_0 \text{ XOR } b_0$$

$$c_1 = a_0 \text{ AND } b_0$$

Adder/Subtractor: 1-bit Adder

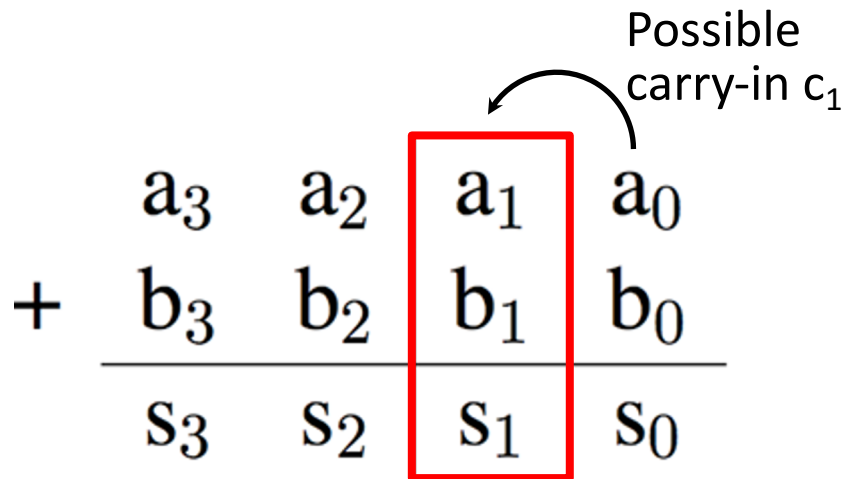



a_i	b_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Here defining XOR of many inputs to be 1 when an *odd* number of inputs are 1

$$\begin{aligned}
 s_i &= \text{XOR}(a_i, b_i, c_i) \\
 c_{i+1} &= \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i
 \end{aligned}$$

Adder/Subtractor: 1-bit Adder

- Circuit Diagrams:**

  


$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$


N x 1-bit Adders \rightarrow N-bit Adder

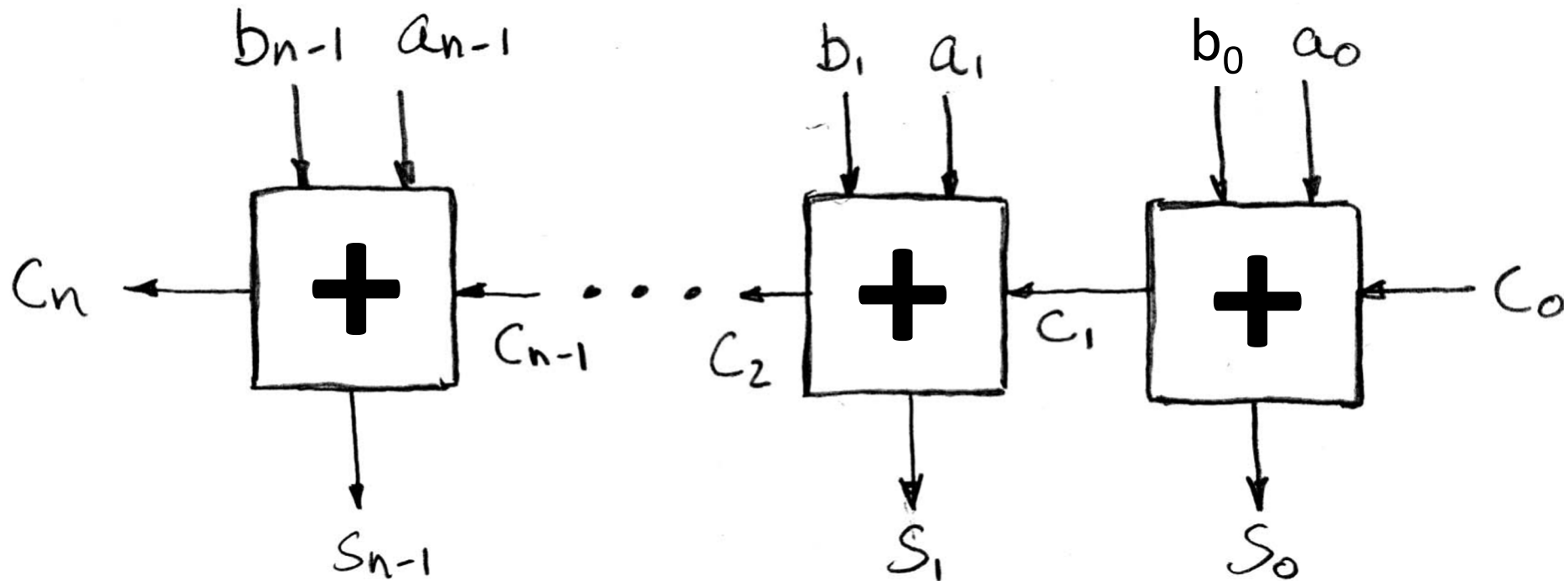- Connect CarryOut_{i-1} to CarryIn_i to chain adders:



Two's Complement Adder/Subtractor

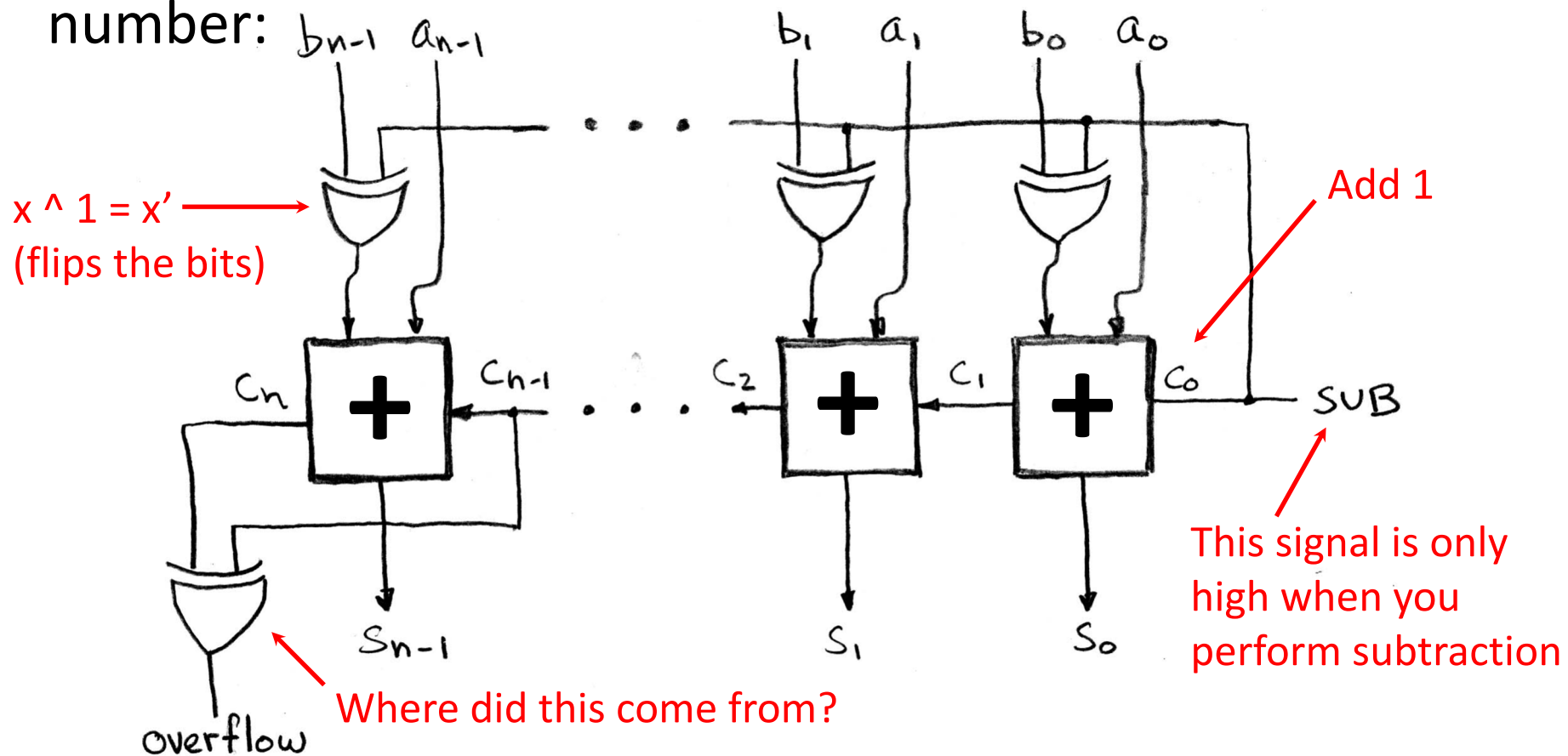- Subtraction accomplished by adding negated number:




Detecting Overflow

- Unsigned overflow
 - On addition, if carry-out from MSB is 1
 - On subtraction, if carry-out from MSB is 0
 - This case is a lot harder to see than you might think
- Signed overflow
 - 1) Overflow from adding “large” positive numbers
 - 2) Overflow from adding “large” negative numbers

Signed Overflow Examples (4-bit)

- Overflow from two positive numbers:
 - $0111 + 0111$, $0111 + 0001$, $0100 + 0100$.
 - Carry-out from the 2nd MSB (but not MSB)
 - $\text{pos} + \text{pos} \neq \text{neg}$
- Overflow from two negative numbers:
 - $1000 + 1000$, $1000 + 1111$, $1011 + 1011$.
 - Carry-out from the MSB (but not 2nd MSB)
 - $\text{neg} + \text{neg} \neq \text{pos}$
- Expression for signed overflow: $C_n \text{ XOR } C_{n-1}$

Simple ALU Schematic

 

Agenda

- Muxes
- Sequential Logic Timing
- Maximum Clock Frequency
- Finite State Machines
- Functional Units
- **Summary**

Bonus Slides

- Logisim Intro

Summary

- Hardware systems are constructed from *Stateless* Combinational Logic and *Stateful* Sequential Logic (includes registers)
- Circuits have a delay to them, and the critical path (longest delay between registers) determines the maximum clock frequency


Non Testable Material

Back to representations


- How do we represent sequential logic?
 - Truth tables could account for history
 - We could do boolean logic with prior state as a variable
- We can also use a new representation:
Finite State Machines

Finite State Machines (FSMs)

 - A convenient way to conceptualize computation over time
- Function can be represented with a *state transition diagram*
- With combinational logic and registers, any FSM can be implemented in hardware!




FSM Overview

 


- An FSM (in this class) is defined by:
 - A set of *states* S (circles)
 - An *initial state* s_0 (only arrow not between states)
 - A *transition function* that maps from the current input and current state to the output and the next state (arrows between states)
- State transitions are controlled by the clock:
 - On each clock cycle the machine checks the inputs and generates a new state (could be same) and

 Example: 3 Ones FSM

- FSM to detect 3 consecutive 1's in the Input




 States: S0, S1, S2
Initial State: S0
Transitions of form:
 input/output




 Example: 3 Ones FSM

- FSM to detect 3 consecutive 1's in the Input




 Starting state in red
Resulting state in Blue




 Example: 3 Ones FSM

- FSM to detect 3 consecutive 1's in the Input




 Starting state in red
Resulting state in Blue




 Example: 3 Ones FSM

- FSM to detect 3 consecutive 1's in the Input




 Starting state in red
Resulting state in Blue




 Example: 3 Ones FSM

- FSM to detect 3 consecutive 1's in the Input




 Starting state in red
Resulting state in Blue




 Example: 3 Ones FSM

- FSM to detect 3 consecutive 1's in the Input




 Starting state in red
Resulting state in Blue




 Example: 3 Ones FSM

- FSM to detect 3 consecutive 1's in the Input




 Starting state in red
Resulting state in Blue




 Example: 3 Ones FSM

- FSM to detect 3 consecutive 1's in the Input




 Starting state in red
Resulting state in Blue




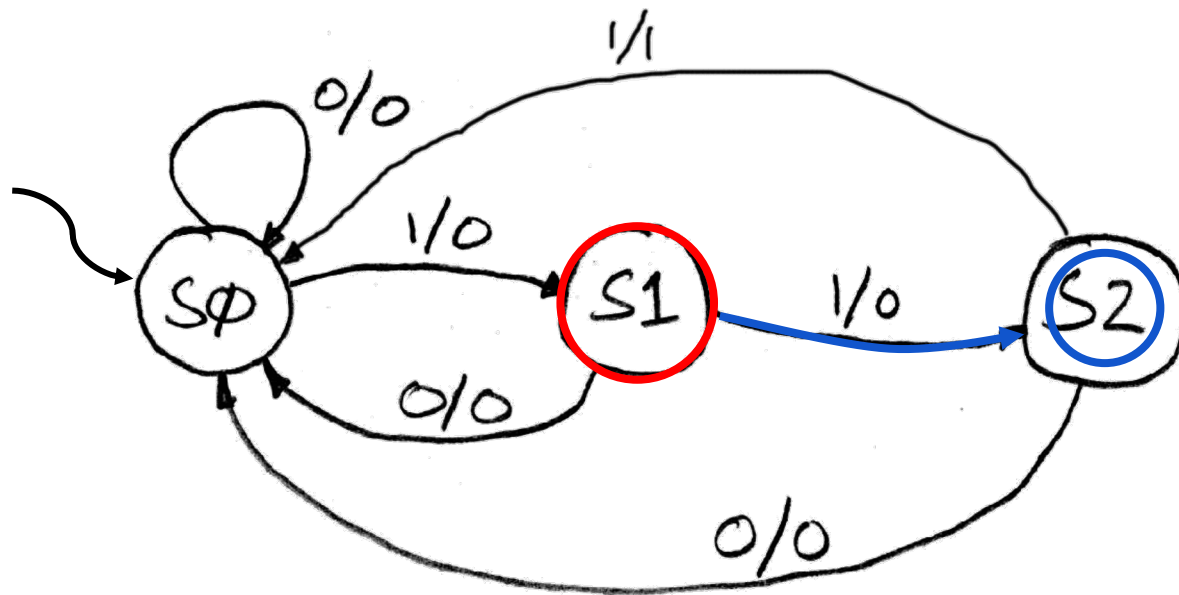Example: 3 Ones FSM

- FSM to detect 3 consecutive 1's in the Input




 Starting state in red
Resulting state in Blue




 Example: 3 Ones FSM

- FSM to detect 3 consecutive 1's in the Input




 Starting state in red
Resulting state in Blue




Hardware Implementation of FSM

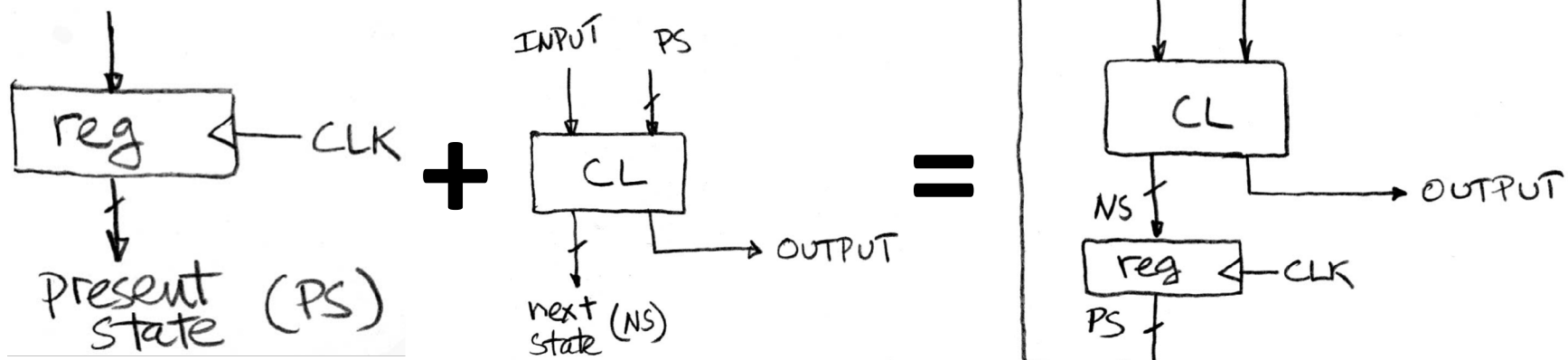- Register holds a representation of the FSM's state
 - Must assign a *unique* bit pattern for each state
 - Output is *present/current state* (PS/CS)
 - Input is *next state* (NS)
- Combinational Logic implements transition function (state transitions + output)



FSM: Combinational Logic

 - Read off transitions into Truth Table!
 - **Inputs:** Current State (CS) and Input (In)
 - **Outputs:** Next State (NS) and Output (Out)



CS	In	NS	Out
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1

Unspecified Output Values

- Our FSM has only 3 states
 - 2 entries in truth table are undefined/unspecified
- Use symbol 'X' to mean it can be either a 0 or 1
 - Make choice to simplify final expression
 - Any choice is correct

CS	In	NS	Out
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1
11	0	XX	X
11	1	XX	X

3 Ones FSM in Hardware

- 2-bit **Register** needed for state
- **CL:** $NS_1 = CS_0In$, $NS_0 = \neg CS_1\neg CS_0In$, $Out = CS_1In$

