

# Digital Logic - Combinational



# Synchronous Digital Systems (SDS)

*Hardware of a processor, such as a RISC-V processor, is an example of a Synchronous Digital System*

## *Synchronous:*

- All operations coordinated by a central clock
  - “Heartbeat” of the system! (processor frequency)

## *Digital:*

- Represent all values with two discrete values
- Electrical signals are treated as 1's and 0's
  - 1 and 0 are complements of each other
- High/Low voltage for True/False, 1/0


# Type of Circuits

- *Digital Systems* consist of two basic types of circuits:
  - Combinational Logic (CL)
    - Output is a function of the inputs only, not the history of its execution
    - e.g. circuits to add A, B (ALUs)
  - Sequential Logic (SL)
    - Circuits that “remember” or store information
    - a.k.a. “State Elements”
    - e.g. memory and registers (Registers)

# Logic Gates (1/2)

- Special names and symbols:

**NOT**

 

$a$	$c$
0	1
1	0

**AND**



$a$	$b$	$c$
0	0	0
0	1	0
1	0	0
1	1	1

**OR**



$a$	$b$	$c$
0	0	0
0	1	1
1	0	1
1	1	1

# Logic Gates (2/2)

Inverted versions are easier to implement in CMOS

**NAND**



a	b	c
0	0	1
0	1	1
1	0	1
1	1	0

**NOR**




a	b	c
0	0	1
0	1	0
1	0	0
1	1	0

**XOR**



a	b	c
0	0	0
0	1	1
1	0	1
1	1	0

# Combining Multiple Logic Gates

 


**(NOT(A AND B)) AND (A OR (NOT B AND C))**

# Agenda

- **Combinational Logic**
  - Combinational Logic Gates
  - **Truth Tables**
  - Boolean Algebra
  - Circuit Simplification

# General Form

 

A	B	C	Y
0	0	0	F(0,0,0)
0	0	1	F(0,0,1)
0	1	0	F(0,1,0)
0	1	1	F(0,1,1)
1	0	0	F(1,0,0)
1	0	1	F(1,0,1)
1	1	0	F(1,1,0)
1	1	1	F(1,1,1)

If  $N$  inputs, how many distinct functions  $F$  do we have?


Function maps each row to 0 or 1,  
so  **$2^N$  possible functions**

# More Complicated Truth Tables

## 3-Input Majority

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

## 2-bit Adder

 

How many rows?

A		B		C		
$a_1$	$a_0$	$b_1$	$b_0$	$c_2$	$c_1$	$c_0$
			.			
			.			
			.			

# Agenda

- **Combinational Logic**
  - Combinational Logic Gates
  - Truth Tables
  - **Boolean Algebra**
  - Circuit Simplification

# Boolean Algebra

- Represent inputs and outputs as variables
    - Each variable can only take on the value 0 or 1
  - Overbar or  $\bar{\phantom{A}}$  is NOT: “logical complement”
    - e.g. if A is 0,  $\bar{A}$  is 1. If A is 1, then  $\bar{A}$  is 0
  - Plus (+) is 2-input OR: “logical sum”
  - Product ( $\cdot$ ) is 2-input AND: “logical product”
    - All other gates and logical expressions can be built from combinations of these
- $\bar{A}B + A\bar{B} == (\text{NOT}(A \text{ AND } B)) \text{ OR } (A \text{ AND NOT } B)$

← For slides,  
will use  $\bar{A}$

# Laws of Boolean Algebra

These laws allow us to perform simplification:

$x \cdot \bar{x} = 0$	$x + \bar{x} = 1$	complementarity
$x \cdot 0 = 0$	$x + 1 = 1$	laws of 0's and 1's
$x \cdot 1 = x$	$x + 0 = x$	identities
$x \cdot x = x$	$x + x = x$	idempotent law
$x \cdot y = y \cdot x$	$x + y = y + x$	commutativity
$(xy)z = x(yz)$	$(x + y) + z = x + (y + z)$	associativity
$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$	distribution
$xy + x = x$	$(x + y)x = x$	uniting theorem
$\bar{x}y + x = x + y$	$(\bar{x} + y)x = xy$	uniting theorem v.2
$\overline{x \cdot y} = \bar{x} + \bar{y}$	$\overline{x + y} = \bar{x} \cdot \bar{y}$	DeMorgan's Law

# Agenda


- **Muxes**
- Sequential Logic Timing
- Maximum Clock Frequency
- Finite State Machines
- Functional Units
- Summary

## Bonus Slides

- Logisim Intro
 
# Data Multiplexor

- Multiplexor (“MUX”) is a *selector*
  - Place one of multiple inputs onto output (N-to-1)
- Shown below is an n-bit 2-to-1 MUX
  - Input S selects between two inputs of n bits each




Represents that  
this wire has n bits

This input is passed  
to output if selector  
bits match shown  
value

# Implementing a 1-bit 2-to-1 MUX

- Schematic:**

 


- Truth Table:**

s	a	b	c
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- Boolean Algebra:**


$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$

- Circuit Diagram:**

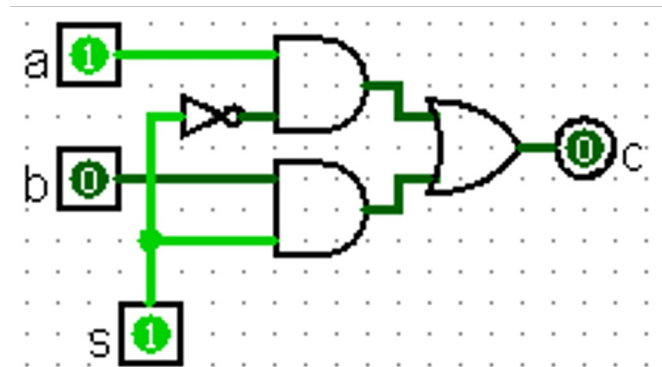

# 1-bit 4-to-1 MUX (1/2)

- **Schematic:**

 


- **Truth Table:** How many rows?  $2^6$
- **Boolean Expression:**


$$e = \neg s_1 \neg s_0 a + \neg s_1 s_0 b + s_1 \neg s_0 c + s_1 s_0 d$$
 
# 1-bit 4-to-1 MUX (2/2)

- Can we leverage what we've previously built?
  - Alternative hierarchical approach:



# Circuit Simplification

 


1) original circuit (Transistors and/or Gates)

$$y = ((ab) + a) + c$$

2) equation derived from original circuit

$$\begin{aligned} &\downarrow \\ &= ab + a + c \\ &\downarrow \\ &= a(b + 1) + c \\ &= a(1) + c \\ &= a + c \end{aligned}$$


3) algebraic simplification

 

4) simplified circuit

# Circuit Simplification Example (2/4)

- Simplify the following circuit:

 

- Start from left, propagate signals to the right

Arrive at  $D = \neg(AB)(A + \neg C)$

# Circuit Simplification Example (3/4)

- Simplify Expression:

$$D = \neg(AB)(A + \neg BC)$$

$$= (\neg A + \neg B)(A + \neg BC)$$

DeMorgan's

$$= \neg AA + \neg A\neg BC + \neg BA + \neg B\neg BC$$

Distribution

$$= 0 + \neg A\neg BC + \neg BA + \neg B\neg BC$$

Complementarity

$$= \neg A\neg BC + \neg BA + \neg BC$$

Idempotent Law

$$= (\neg A + 1)\neg BC + \neg BA$$

} Which of these  
is "simpler"?


# Circuit Simplification Example (4/4)

- Draw out final circuit:

$$- D = \underbrace{-BC}_5 + \underbrace{-BA}_3 = \underbrace{-B(A + C)}_3$$

How many gates do we need for each?

- Simplified Circuit:

 

- Reduction from 6 gates to 3!

# Digital Logic - Sequential



# Accumulator Example

An example of why we would need sequential logic




Want:  $S=0;$   
 for  $X_1, X_2, X_3$  over time...  

$$S = S + X_i$$

Assume:

- Each  $X$  value is applied in succession, one per cycle
- The sum since time 1 (cycle) is present on  $S$

# Second Try: How About This?

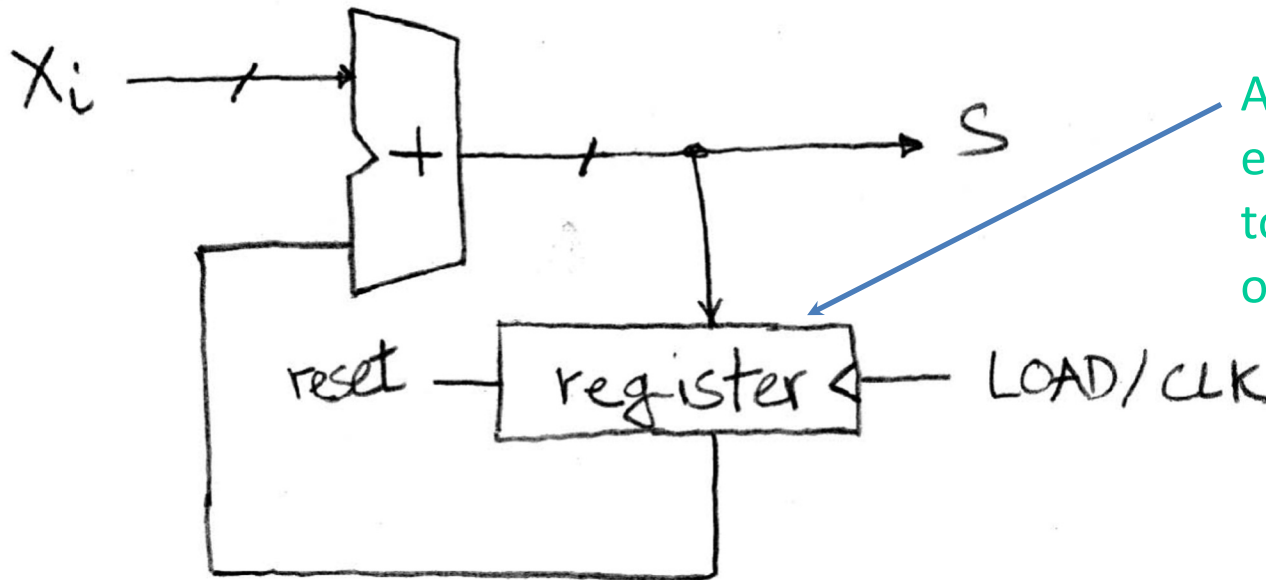

A *Register* is the state element that is used here to hold up the transfer of data to the adder


# Uses for State Elements

- Place to store values for some amount of time:
  - Register files (like in RISC-V)
  - Memory (caches and main memory)
- *Help control flow of information between combinational logic blocks*
  - State elements are used to hold up the movement of information at the inputs to combinational logic blocks and allow for orderly passage


# Registers

Same as registers in assembly:

- small memory storage locations

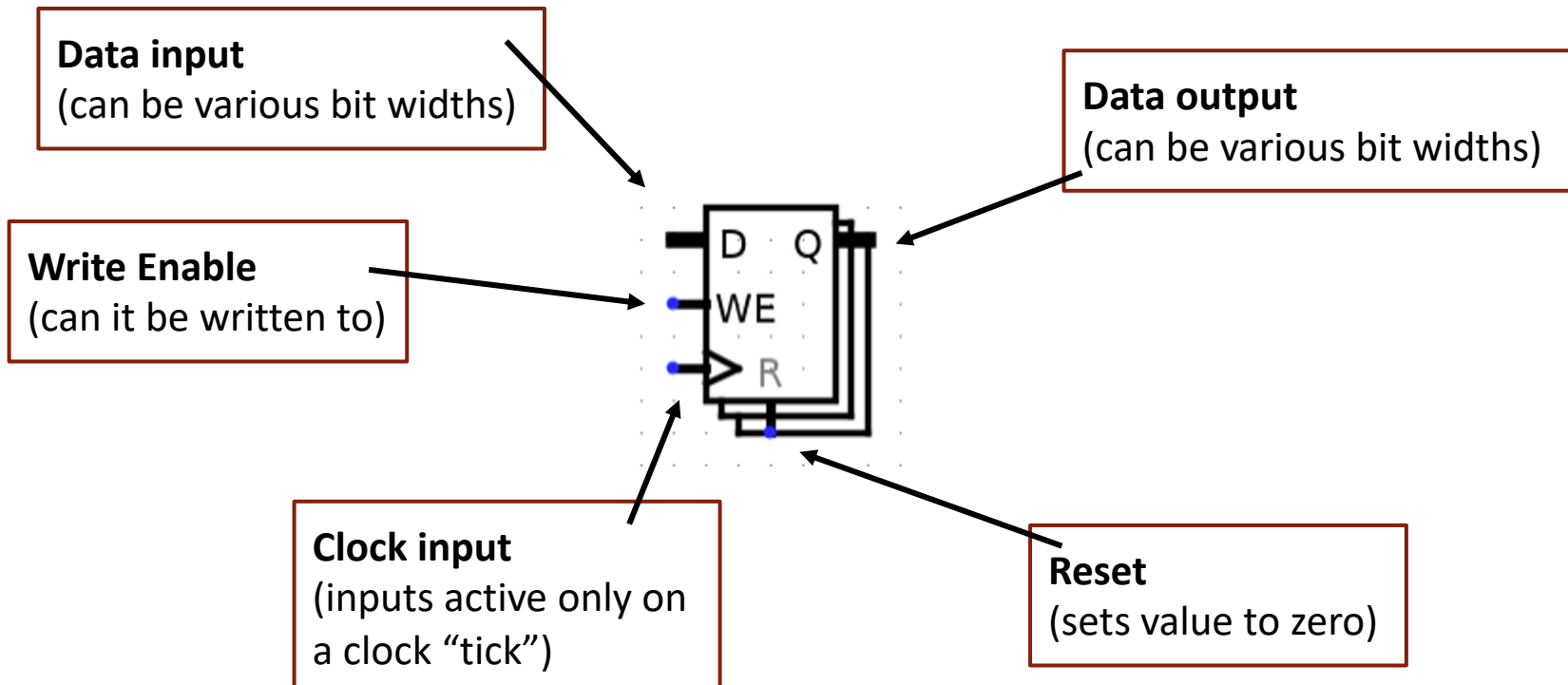

# Signals and Waveforms: Clocks

 


- **Signals** transmitted over wires continuously
- Transmission is effectively instantaneous
  - Implies that any wire only contains one value at any given time

# Review of Timing Terms

- **Clock:** steady square wave that synchronizes system
- **Register:** several bits of state that samples on rising edge of Clock (positive edge-triggered); also has RESET
- **Setup Time:** when input must be stable *before* Clock trigger
- **Hold Time:** when input must be stable *after* Clock trigger
- **Clock-to-Q Delay:** how long it takes output to change from Clock trigger

# Model for Synchronous Systems

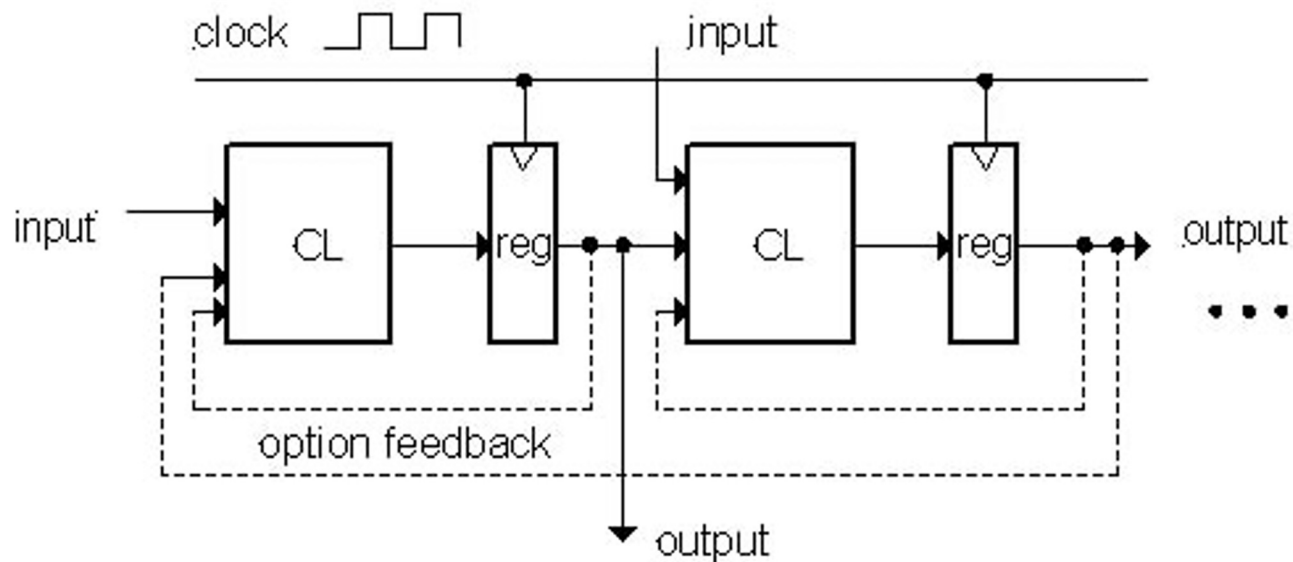

- Combinational logic blocks separated by registers
  - Clock signal connects only to sequential logic elements
  - Feedback is optional depending on application
- How do we ensure proper behavior?
  - How fast can we run our clock?


# When can the input change?

- Needs to be stable for duration of setup time + hold time
- Often unstable until at least clock-to-q time has passed
  - Because register output isn't ready yet
- Needs to account for all combinational logic delay too

# Maximum Clock Frequency

- What is the max frequency of this circuit?
  - Limited by how much time needed to get correct Next State to Register ( $t_{setup}$  constraint)

Assumes Max Delay > Hold Time

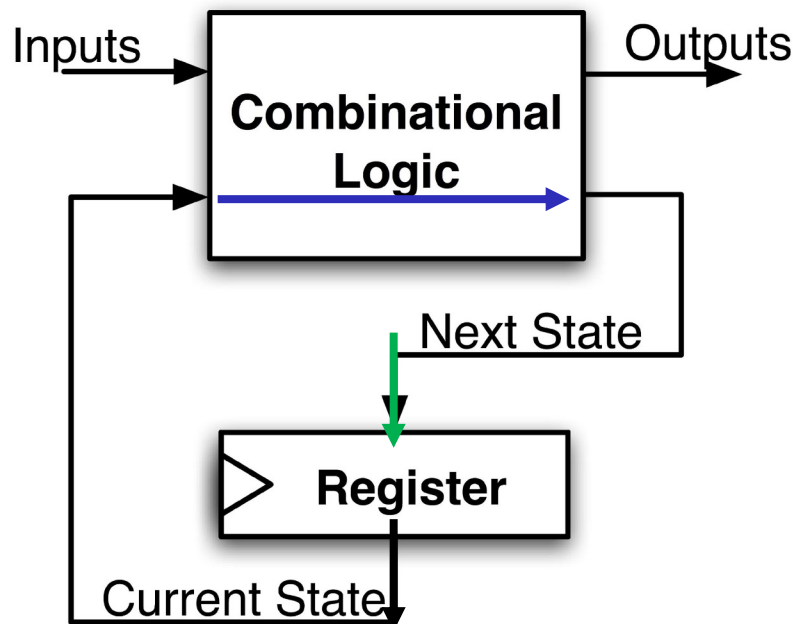


$$\begin{aligned} \text{Max Delay} &= \text{CLK-to-Q Delay} \\ &+ \text{CL Delay} \\ &+ \text{Setup Time} \end{aligned}$$

$$\begin{aligned} \text{Min Period} &= \text{Max Delay} \\ \text{Max Freq} &= 1/\text{Min Period} \end{aligned}$$
 
# The Critical Path

- The *critical path* is the longest delay between *any* two registers in a circuit
- The clock period must be *longer* than this critical path, or the signal will not propagate properly to that next register




# How do we go faster?

## Pipelining!


- Split operation into smaller parts and add a register between each one.
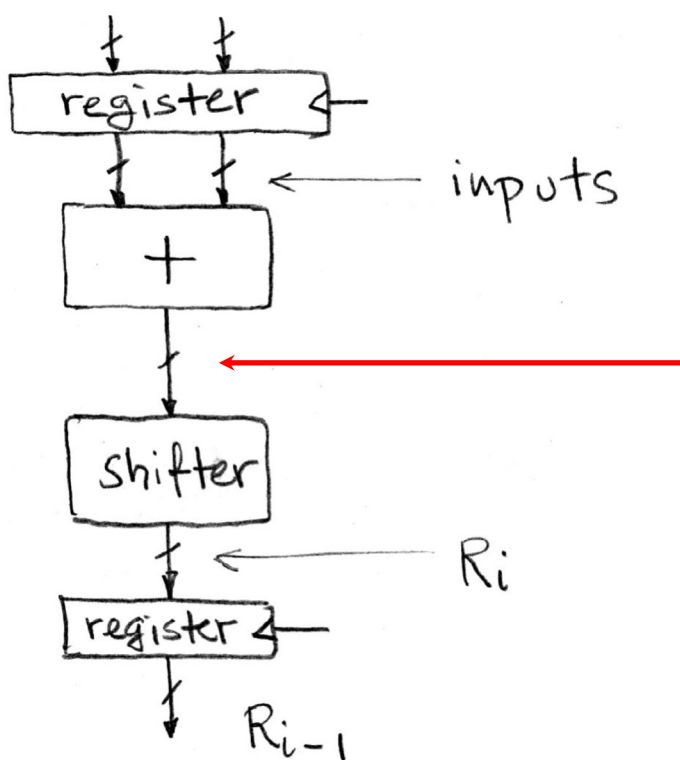
# Pipelining and Clock Frequency (1/2)



- Clock period limited by propagation delay of adder and shifter
  - Add an extra register to reduce the critical path!



## Timing:

 

# Pipelining and Clock Frequency (2/2)

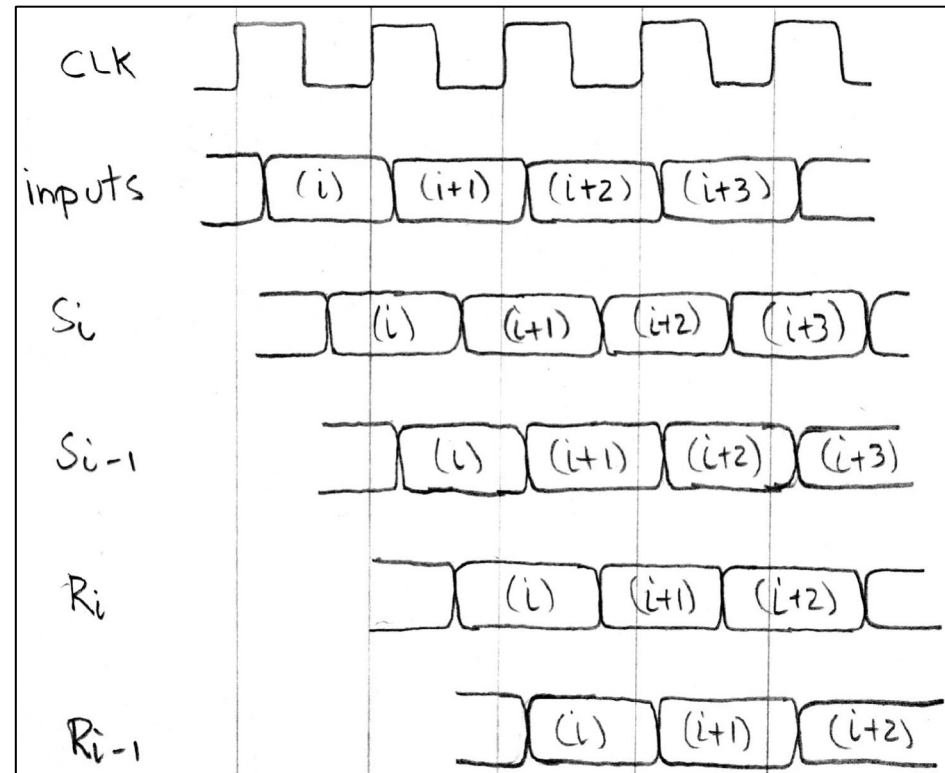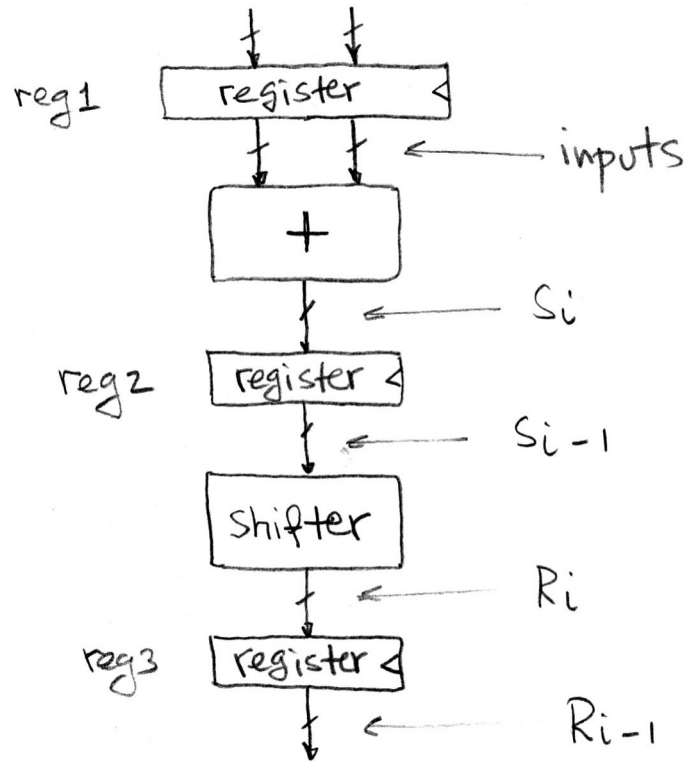

- Reduced critical path  $\rightarrow$  allows higher clock freq.
- Extra register  $\rightarrow$  extra (shorter) cycle to produce first output

# Pipelining Basics

- By adding more registers, break path into shorter “stages”
  - Aim is to reduce critical path
  - Signals take an additional clock cycle to propagate through *each* stage
- New critical path must be calculated
  - Affected by placement of new pipelining registers
  - Faster clock rate → higher throughput (outputs)
  - More stages → higher startup latency
- **Pipelining tends to improve performance**
  - More on this (and application to CPUs) later